

JEE MAIN

CURRENT ELECTRICITY FORMULAE

Now that's how you REVISE

-Mohit Goenka, IIT Kharagpur

List of Content on Eduniti YouTube Channel:

1. PYQs Video Solution Topic Wise:
 - (a) JEE Main 2018/2020/2021 Feb & March
2. Rank Booster Problems for JEE Main
3. Part Test Series for JEE Main
4. JEE Advanced Problem Solving Series
5. Short Concept Videos
6. Tips and Tricks Videos
7. JEE Advanced PYQs

.....and many more to come



EDUNITI




Eduniti for Physics

1. CHARGE FLOW


$$Q_{\text{flown}} = \int_{t_1}^{t_2} i(t) dt$$

Ex: $i(t) = 2 \sin 50\pi t$

$$i(t) = 3t^2$$

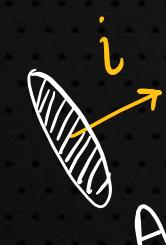

2. IMPORTANT CURRENT PARAMETERS

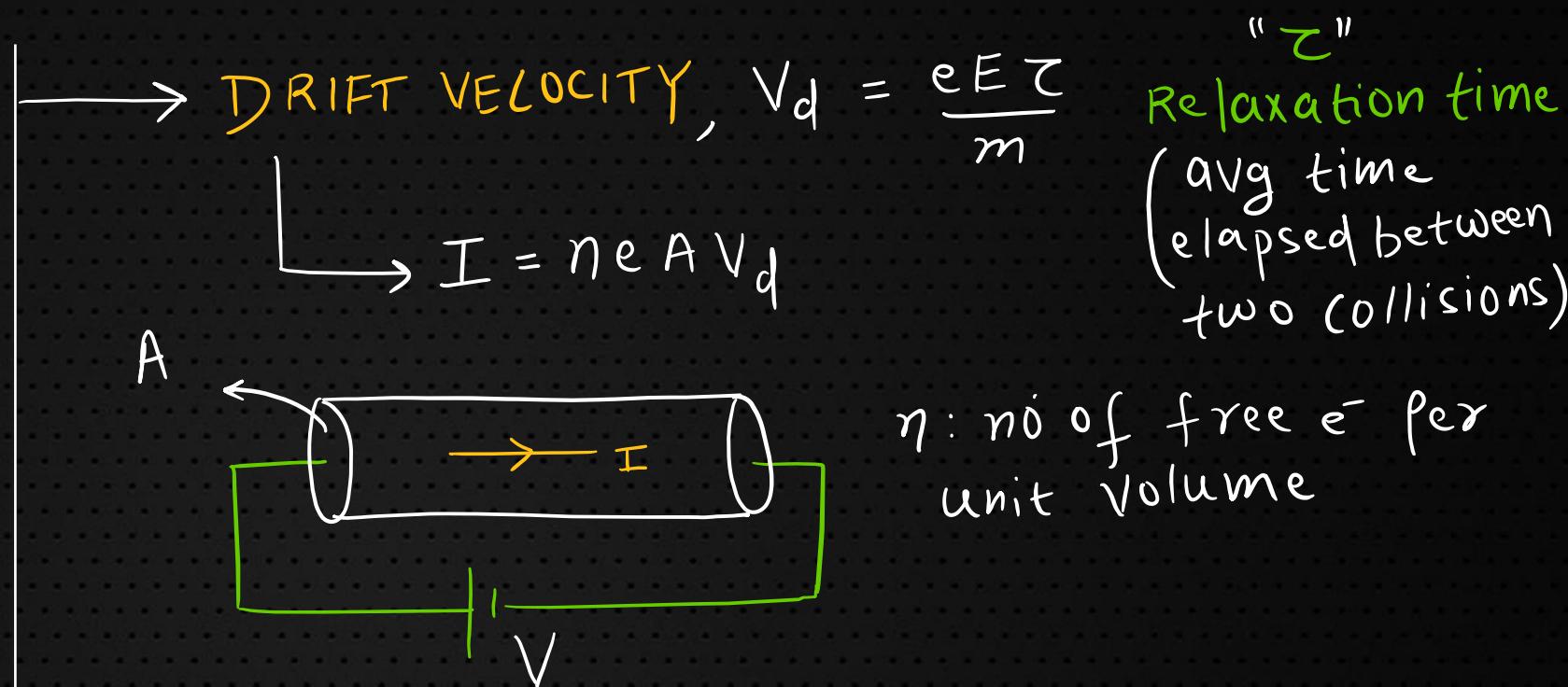

$$\text{MOBILITY}, \mu = \frac{v_d}{E} = \frac{eE\tau/m}{E} = \frac{e\tau}{m}$$

$$\text{CURRENT DENSITY}, J = I/A \Rightarrow I = \vec{J} \cdot \vec{A}$$

$$E = \rho J$$

ρ : Resistivity



3. RESISTANCE $(R = \frac{m}{ne^2\tau} \frac{l}{A})$, ohm (Ω)

ρ : resistivity, $\sigma = \frac{1}{\rho}$

R DEPENDS ON:

$$\begin{array}{l} R \propto l \\ R \propto 1/A \end{array}$$

If temperature increases, Resistance also increases. $\left\{ \rho = \frac{m}{ne^2\tau}, \text{ If } T \uparrow \Rightarrow \tau \downarrow \Rightarrow \rho \uparrow \right. \\ \Rightarrow R \uparrow \right.$

For small variation in temp°

$$R_{T_2} = R_{T_1} (1 + \alpha \Delta T),$$

$$\rho_{T_2} = \rho_{T_1} (1 + \alpha \Delta T)$$

FOR SEMICONDUCTORS

$$\left. \begin{array}{l} \text{If } T \uparrow \Rightarrow \rho \downarrow \\ \Rightarrow R \downarrow \end{array} \right.$$

(on $\tau \uparrow$, $n \uparrow$
dominating \downarrow in τ)



Source :
NCERT

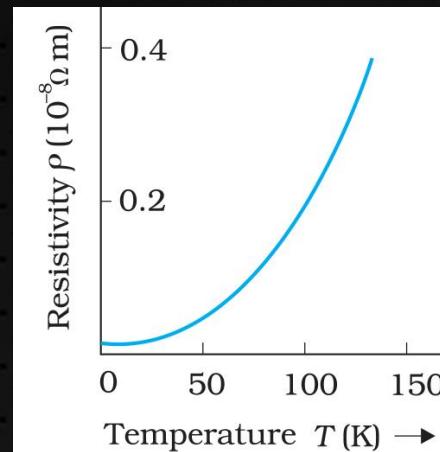


FIGURE 3.9
Resistivity ρ_T of
copper as a function
of temperature T .

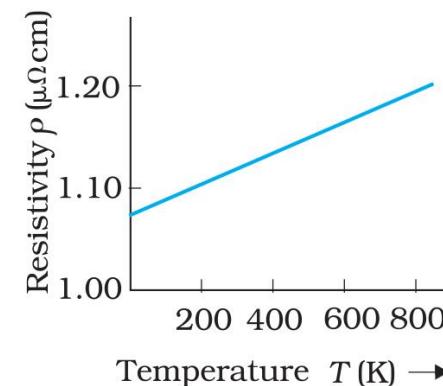


FIGURE 3.10 Resistivity
 ρ_T of nichrome as a
function of absolute
temperature T .


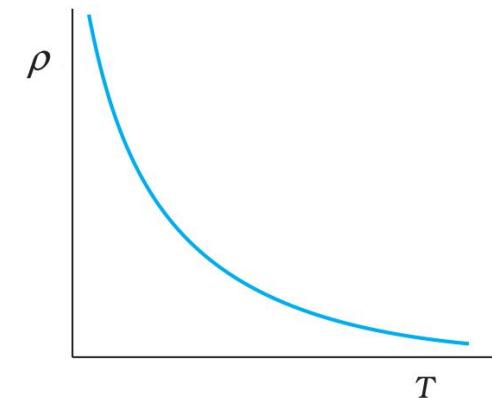


FIGURE 3.11
Temperature dependence
of resistivity for a typical
semiconductor.

→ Manganin
and
constantan

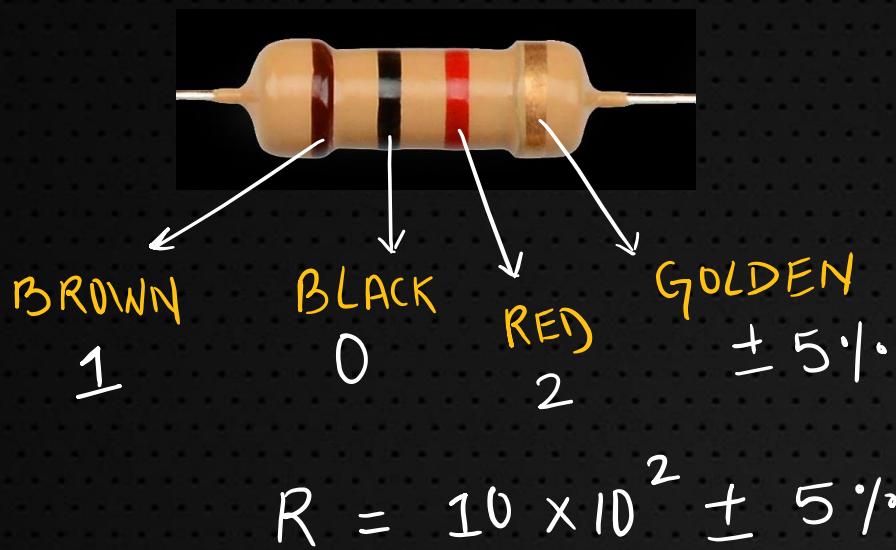


4. COLOUR CODE




Resistor colour codes			
Colour	Number	Multiplier	Tolerance (%)
Black	0	10^0	
Brown	1	10^1	
Red	2	10^2	
Orange	3	10^3	
Yellow	4	10^4	
Green	5	10^5	
Blue	6	10^6	
Violet	7	10^7	
Gray	8	10^8	
White	9	10^9	
Gold		10^{-1}	5
Silver		10^{-2}	10
No colour			20



5. CELL (Emf, Internal Resistance)

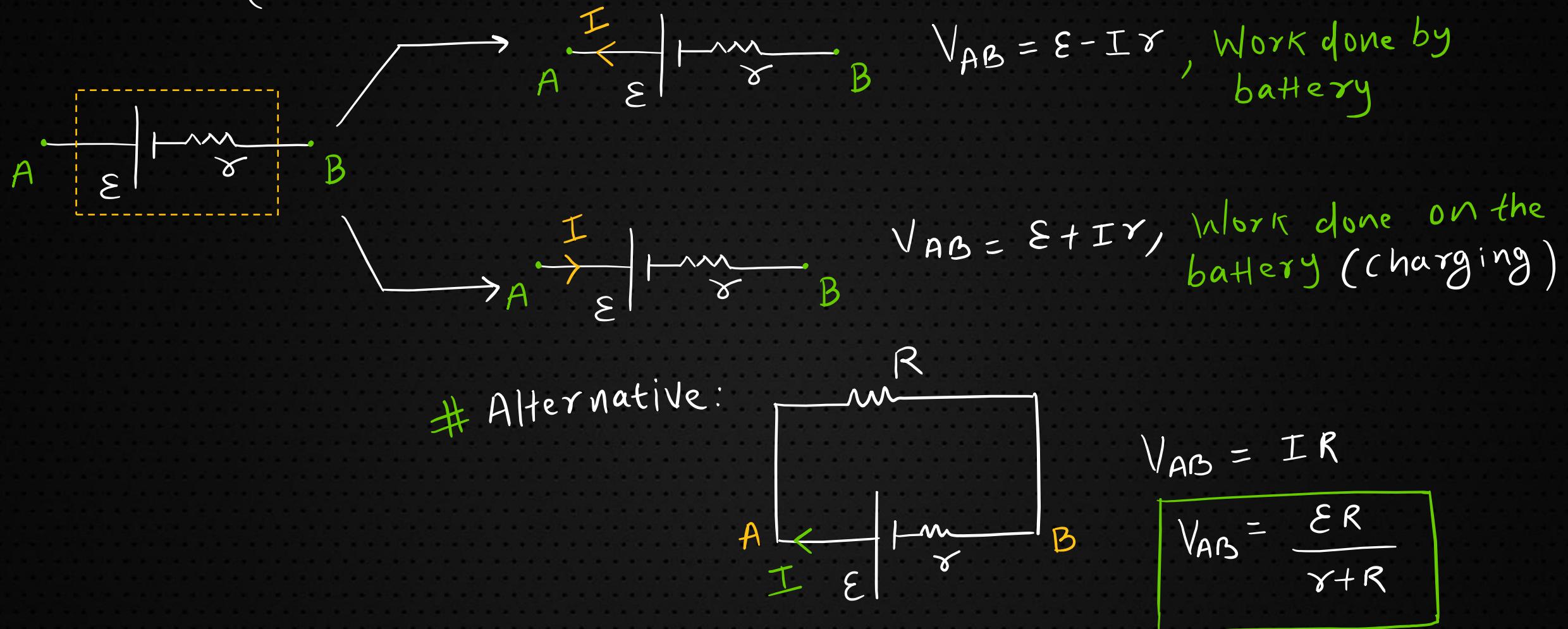

Alternative:

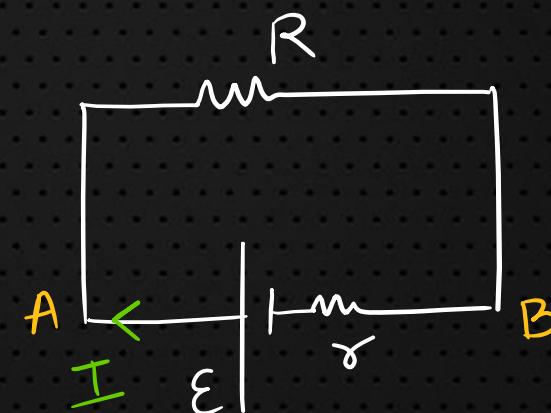


$$V_{AB} = IR$$

$$V_{AB} = \frac{\epsilon R}{r+R}$$




6. COMBINATION OF CELL

SERIES →

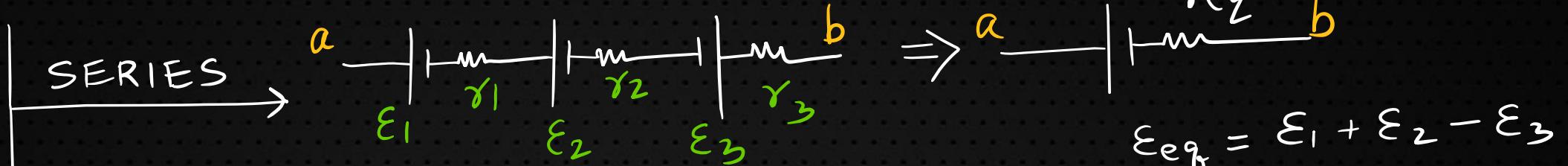

PARALLEL →

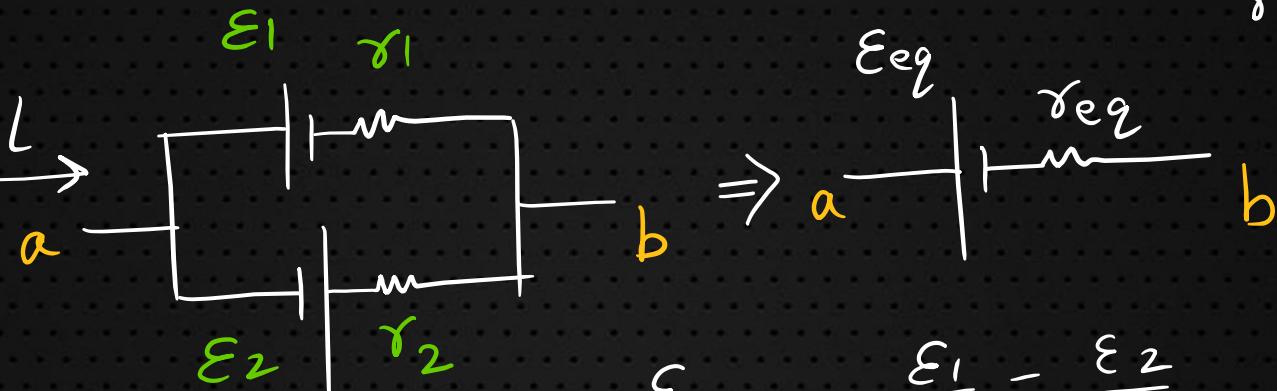

Here we took
 $\begin{array}{c} + \\ | \\ - \end{array}$ as $+\epsilon$


$$\epsilon_{eq} = \frac{\frac{\epsilon_1}{r_1} - \frac{\epsilon_2}{r_2}}{\frac{1}{r_1} + \frac{1}{r_2}}, \quad \frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2}$$




7. KIRCHHOFF's LAW (KVL and KCL)

↓
LOOP RULE ↓ JUNCTION RULE

$$\text{KCL} (\sum i_n = 0)$$

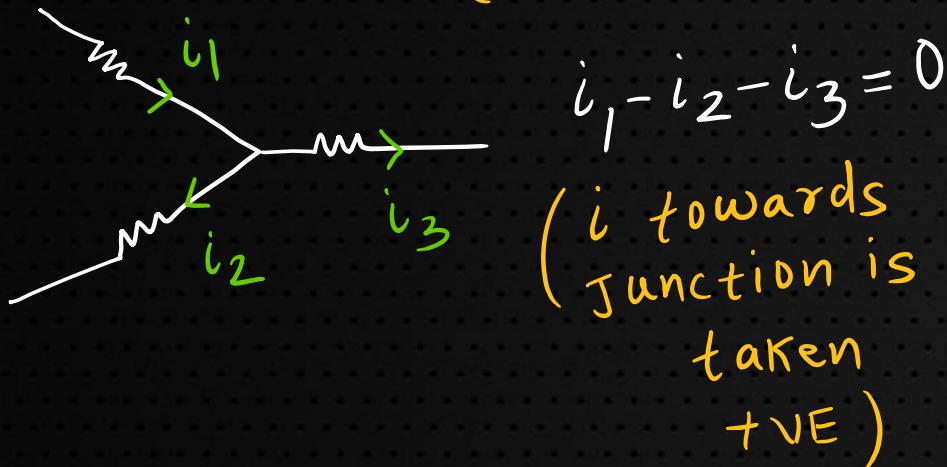
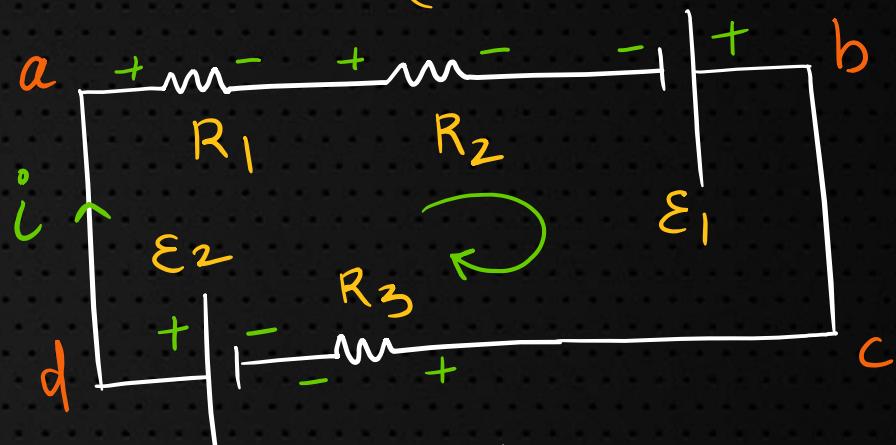
$$\text{KVL } (\sum V_n = 0) \text{ In a Loop}$$



In Loop abcd a

$$iR_1 + iR_2 - \varepsilon_1 + iR_3 - \varepsilon_2 = 0$$



8. CIRCUIT ANALYSIS MORE TECHNIQUES


P.d. distribution



$$\because i \text{ is same} \quad V_1 = \frac{V R_1}{R_1 + R_2}, \\ \Rightarrow V \propto R$$

$$V_2 = \frac{V R_2}{R_1 + R_2}$$

i distribution

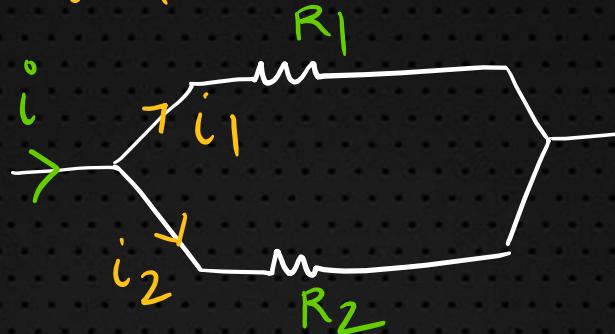


$$\because V \text{ is same} \\ \Rightarrow i \propto 1/R$$

$$i_1 = \frac{i R_2}{R_1 + R_2}$$

$$i_2 = \frac{i R_1}{R_1 + R_2}$$

Point Potential Method

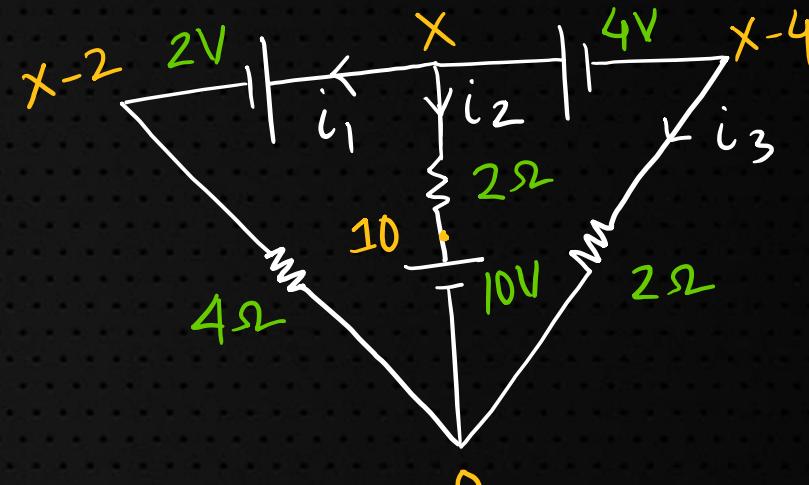

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{X-2}{4} + \frac{X-10}{2} + \frac{X-4}{2} = 0$$

$$X = 6V$$




9. COMBINATION OF RESISTORS

SERIES







$$R_{\text{eq}} = R_1 + R_2$$

PARALLEL

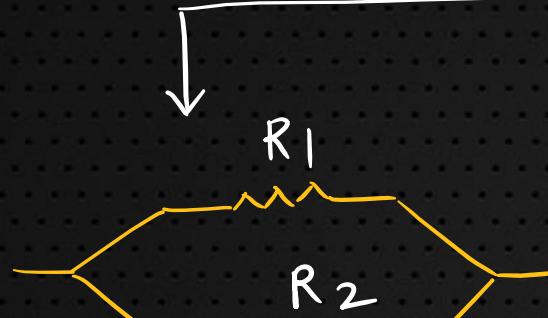


$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

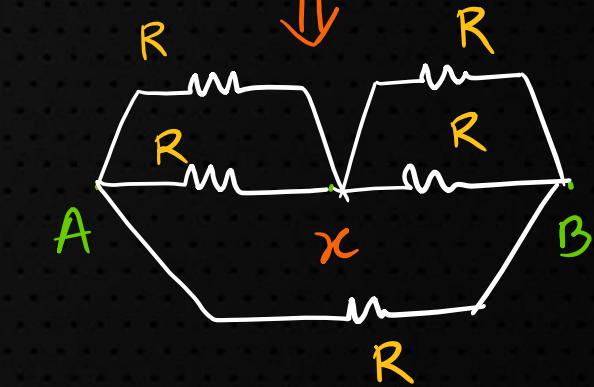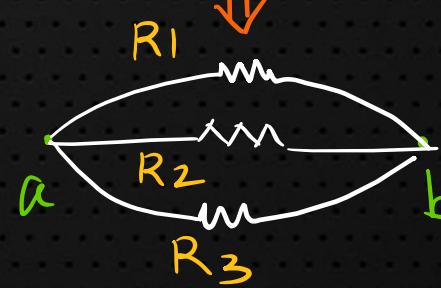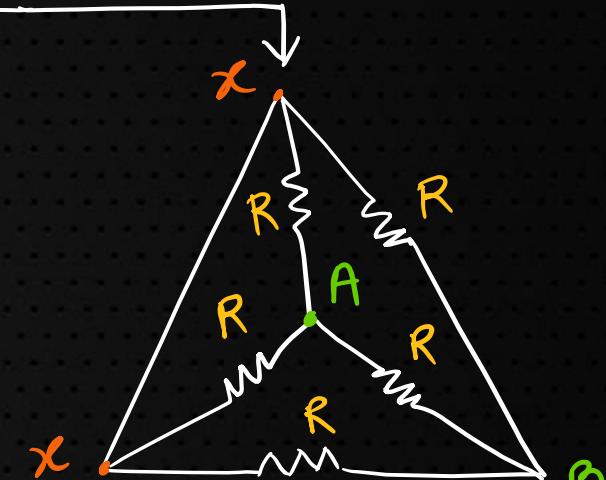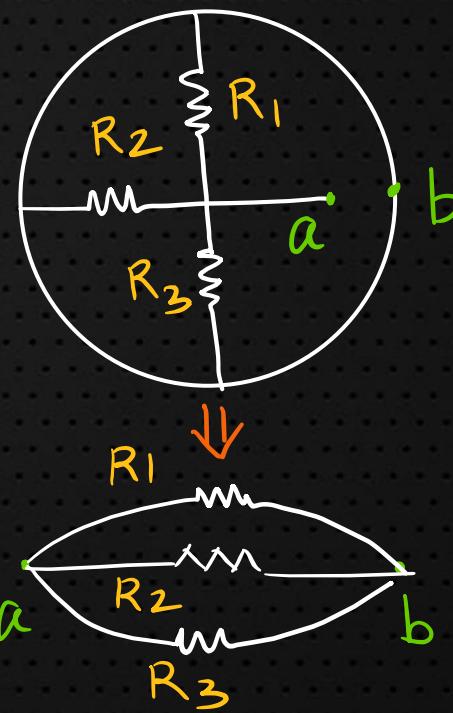
$$\Rightarrow R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$



10. WHEATSTONE BRIDGE (BALANCED)

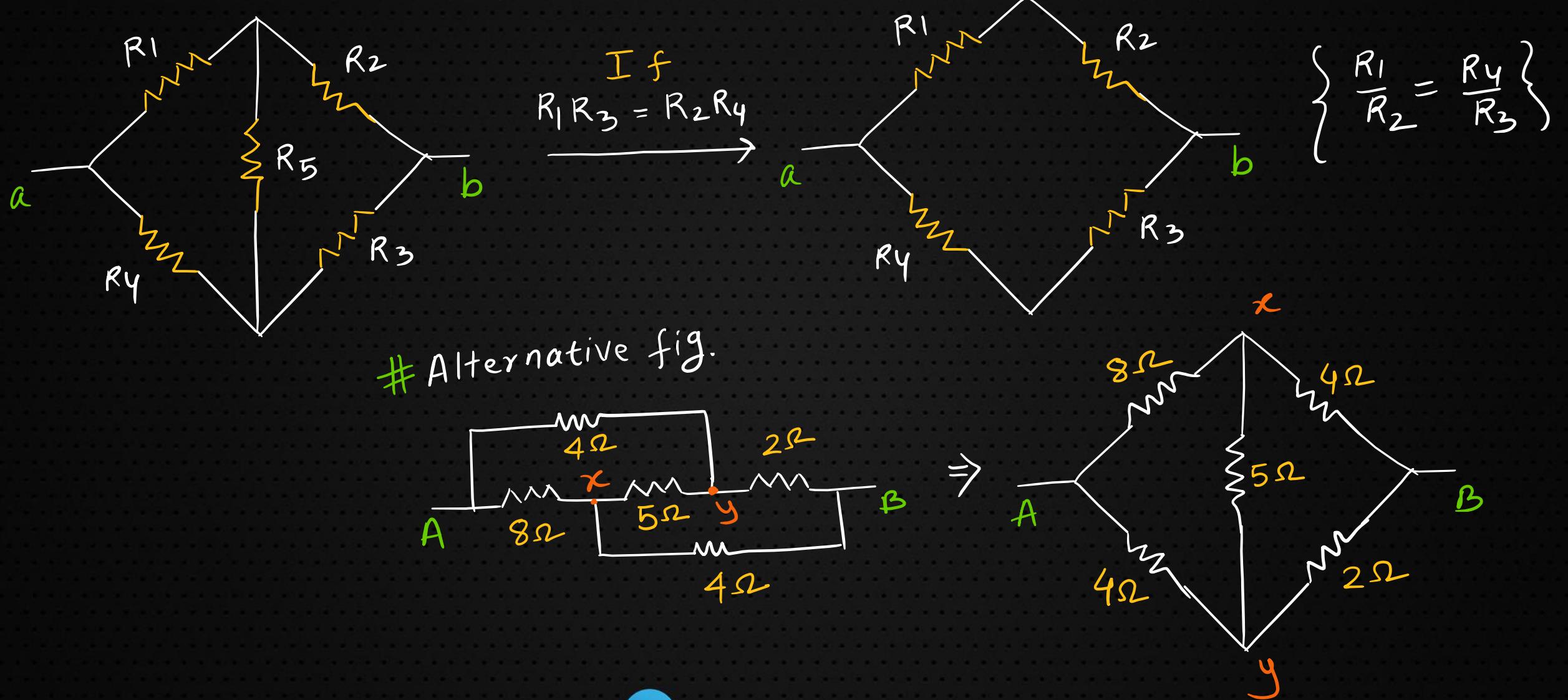



11. CUBE RESISTORS

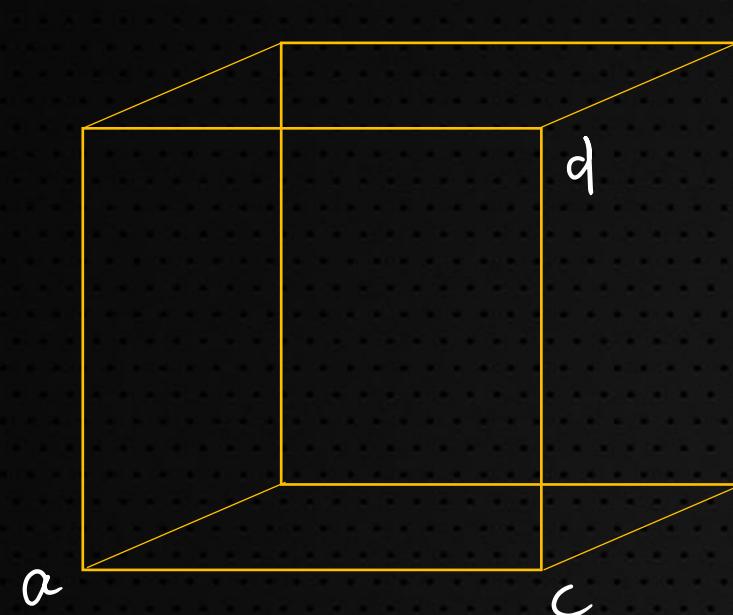

$$R_{eq,ab} = 5R/6 \text{ (body diagonal)}$$

$$R_{eq,ac} = 7R/12 \text{ (edge)}$$
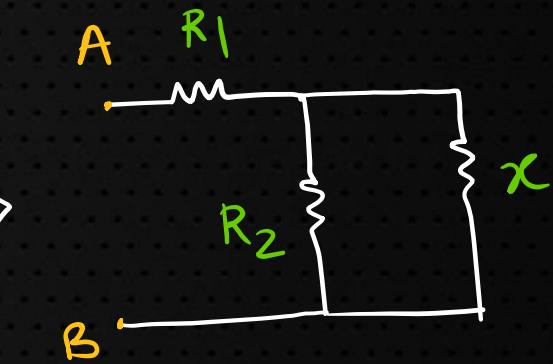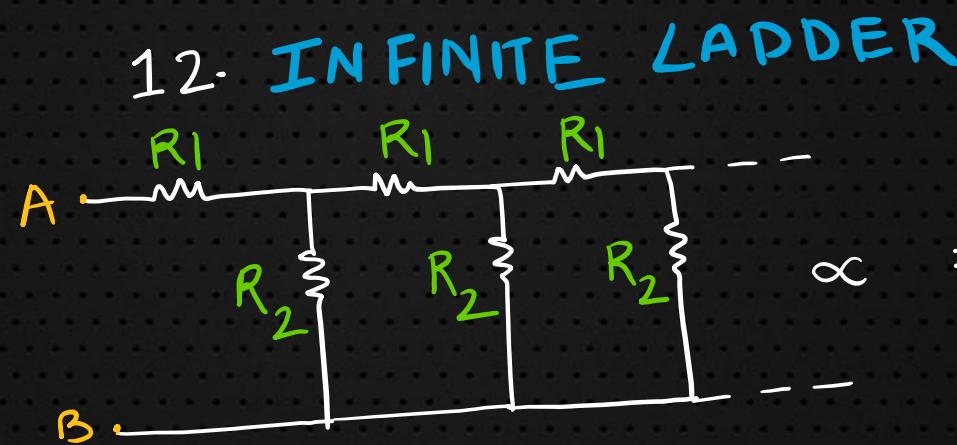
$$R_{eq,ad} = 3R/4 \text{ (face diagonal)}$$



$$R_{AB} = R_1 + \frac{xR_2}{x+R_2}$$

$\downarrow x$



13. THERMAL EFFECT OF CURRENT (JOULES HEATING EFFECT)

↓
CONSTANT CURRENT



$$P = i^2 R = \frac{V^2}{R} = Vi \text{ (Watt)}$$

$$H = i^2 R t = \frac{V^2}{R} t = Vit \text{ (Joules)}$$

↓
Time Varying Current




$$H = \int_{t_1}^{t_2} i^2 R dt$$

$$P_{av} = \frac{\int i^2 R dt}{\int dt}$$

$$\text{Ex: } i(t) = i_0 \sin \omega t$$



14. MAX POWER TRANSFER THEOREM

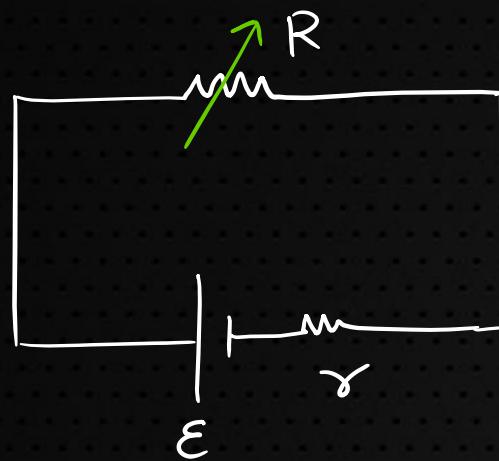

CONDITION :

$$R = r$$

→ for maximum power transfer, external resistance must be equal to internal resistance.

15. CONCEPT OF POWER RATING



BULB

specifications

220V, 50W

Rated Voltage

Rated Power

NOTE:

(i) Means bulb will consume 50W if 220V is across it.

$$(ii) R_{\text{bulb}} = \frac{V^2}{P} = \frac{220^2}{50} = 968\Omega$$

(iii) If $V > 220V$ is across bulb, it will fuse

(iv) More Power \Rightarrow More Bright



16. GALVANOMETER TO AMMETER AND VOLTMETER


(a) AMMETER

→ connected in Series


→ IDEAL AMMETER

has zero resistance

(Practically it has very low resistance)

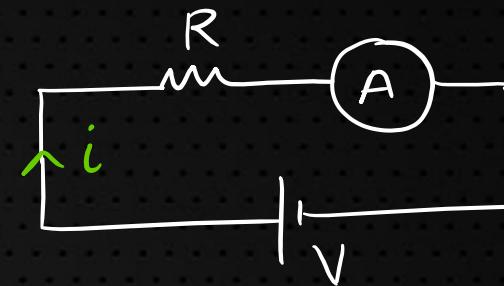

CONVERSION:

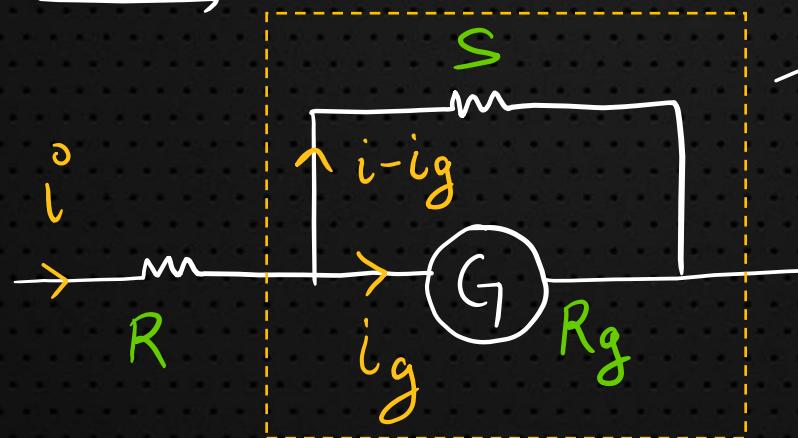

(i) i_g is max current that can pass through G for full deflection

(ii) $S \ll R_g$ (S : shunt)

$$(iii) (i - i_g)S = i_g R_g \Rightarrow i = i_g \left(1 + \frac{R_g}{S}\right)$$



17. GALVANOMETER TO AMMETER AND VOLTMETER



(b) Voltmeter

→ connected in parallel

→ IDEAL VOLTMETER

has infinite Resistance

(Practically it has very resistance)

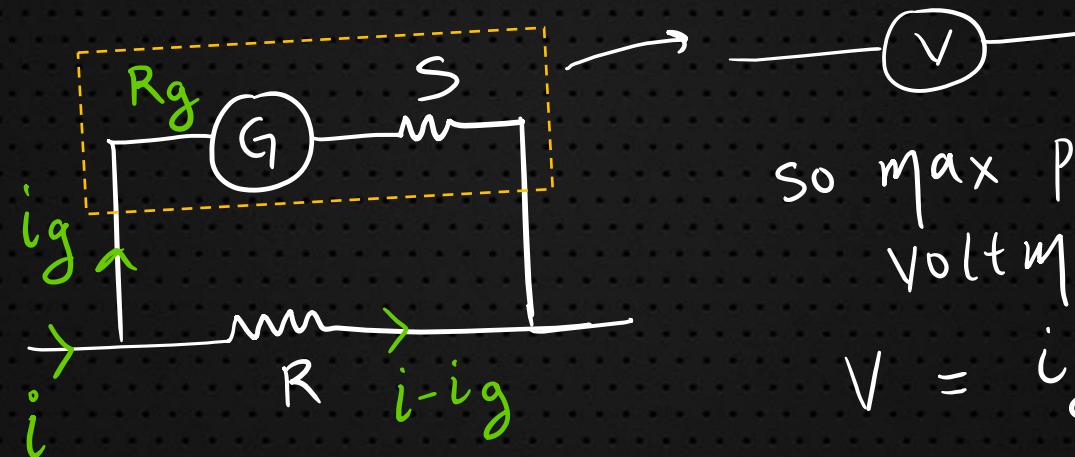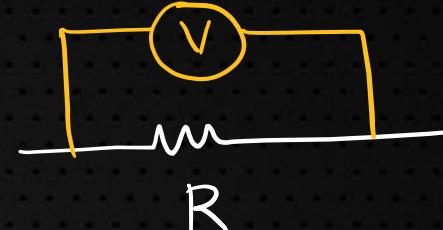

so max p.d. measured by
voltmeter is,


$$V = i_g (R_g + s)$$

↪ i_g : galvanometer current for
full deflection



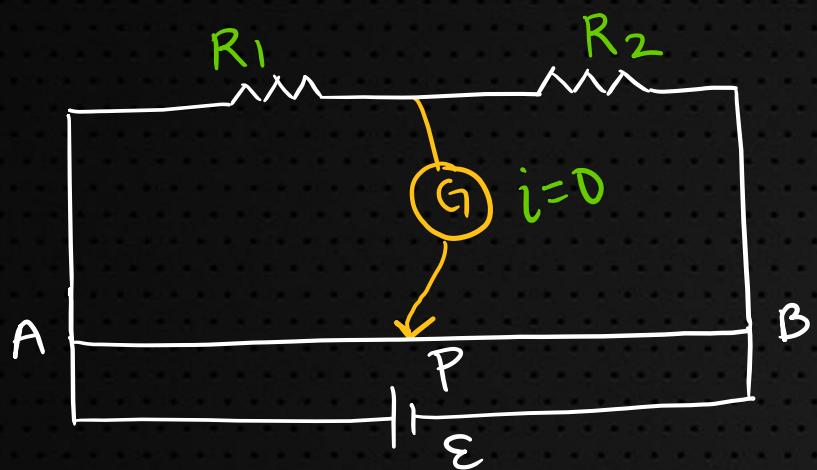18. METER BRIDGE


→ AIM: to find resistance of unknown resistor (R_2)
 → Based on Balanced WHEATSTONE BRIDGE



$$AP = l_1$$

$$BP = l_2$$

P is "Null-Deflection" point.

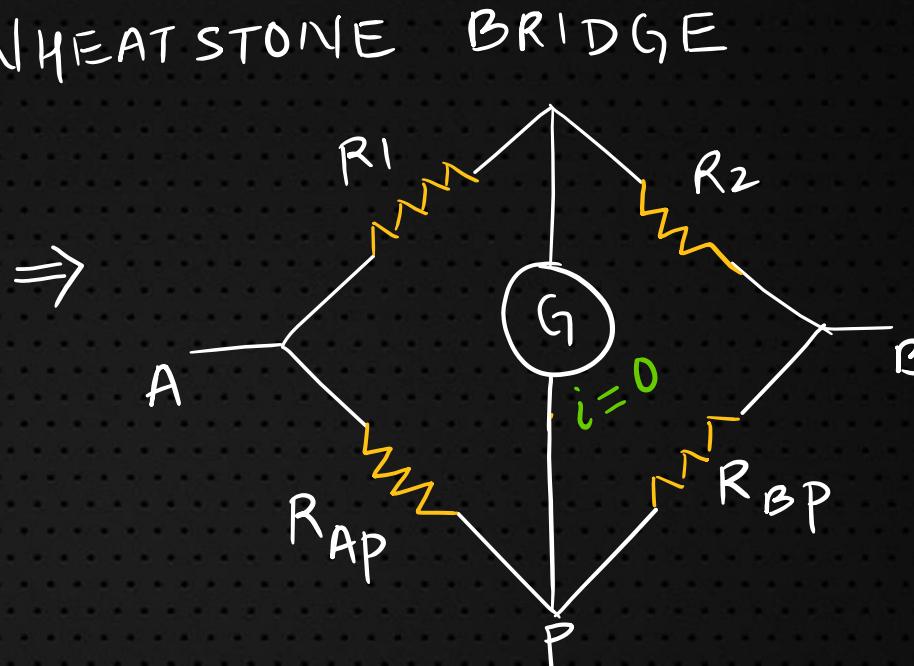

$$\frac{R_1}{R_2} = \frac{R_{AP}}{R_{BP}}$$

$$\boxed{\frac{R_1}{R_2} = \frac{l_1}{l_2}}$$

or

$$R_2 = R_1 \times \frac{l_2}{l_1}$$

Generally $l_1 + l_2 = 100\text{cm}$




19. POTENTIOMETER

→ AIM: To find emf of a cell and its internal resistance

→ Potential gradient (k) : $k = \frac{\text{P.d.}}{l} \text{ V/m}$ (Potential difference per unit length)

(a) FINDING EMF OF A CELL

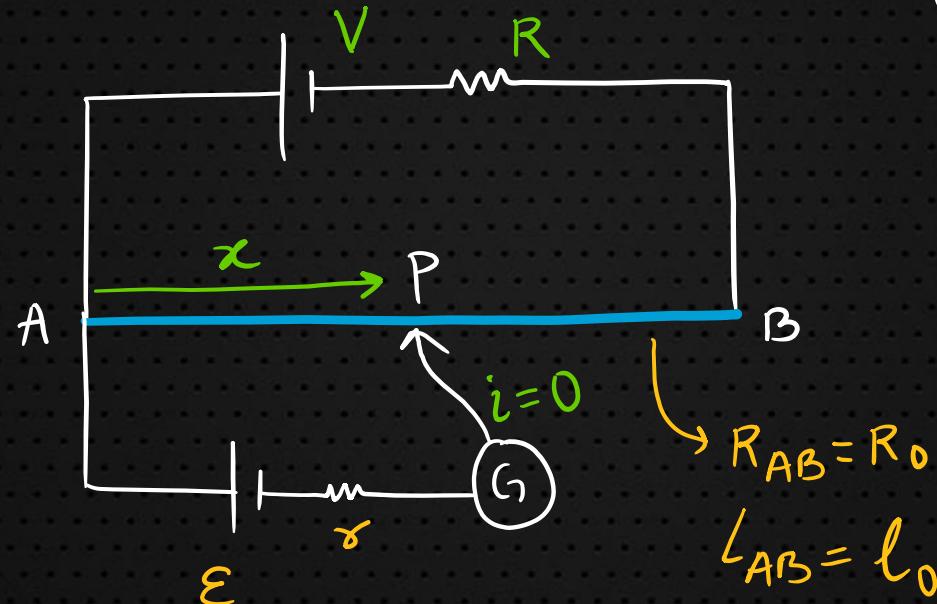

(i) P is null-deflection pt.
or balance pt.

$$(ii) k = V_{AB}/l_0, V_{AB} = \frac{VR_0}{R_0 + R}$$

$$(iii) \epsilon = V_{AP}$$

$$\Rightarrow \boxed{\epsilon = kx}$$

NOTE: MAX value of ϵ that can be measured is
 $E_{\max} = V_{AB}$



(b) FINDING Internal resistance (γ)

(i) When key is open:

(Null deflection at Q)

$$\mathcal{E} = kx_1 \quad \dots \quad (1)$$


(ii) When key is closed

(Null deflection at P)

$$V_{CD} = kx_2$$

$$\Rightarrow \frac{\mathcal{E}R_1}{R_1 + \gamma} = kx_2 \quad \dots \quad (2)$$
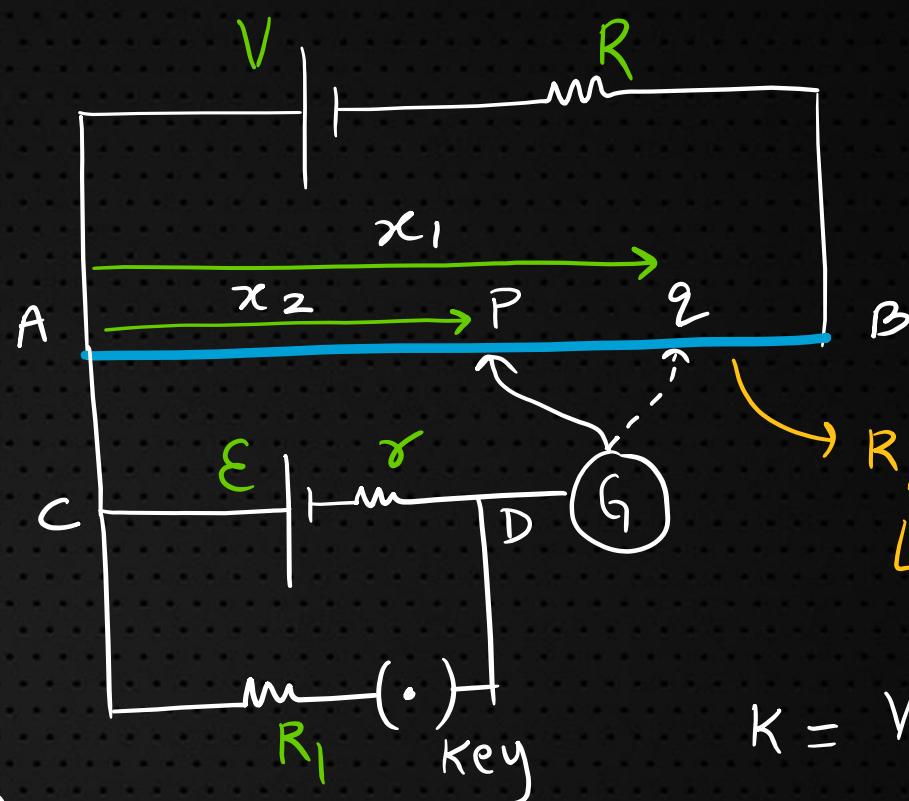
$$(1)/(2) : \frac{R_1 + \gamma}{R_1} = \frac{x_1}{x_2}$$



$$R_{AB} = R_0$$

$$L_{AB} = l_0$$

$$K = V_{AB} / l_0$$

$$= \left(\frac{VR_0}{R+R_0} \right) \frac{1}{l_0}$$

$$\Rightarrow \gamma = R \left(\frac{x_1 - x_2}{x_2} \right)$$

