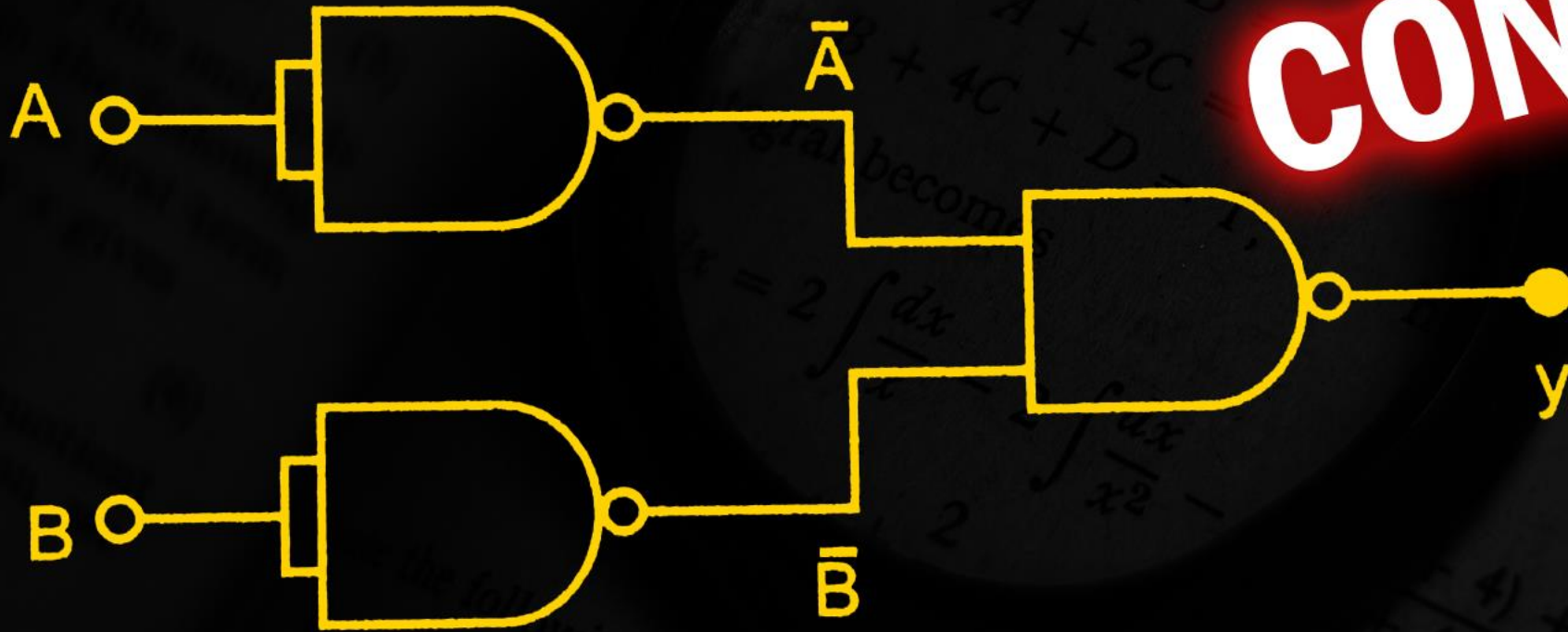


LOGIC GATE

JEE MAIN

Semiconductor -3



CONCEPT
PYQs



by Mohit Goenka, IIT Kharagpur

List of Content on Eduniti YouTube Channel:

1. PYQs Video Solution Topic Wise:
(a) JEE Main 2018/2020/2021 Feb & March
2. Rank Booster Problems for JEE Main
3. Part Test Series for JEE Main
4. JEE Advanced Problem Solving Series
5. Short Concept Videos
6. Tips and Tricks Videos
7. JEE Advanced PYQs
8. Formulae Revision Series

.....and many more to come



Eduniti for Physics

Playlist Link in Description

MODERN PHYSICS - PART 1
FORMULAE
ATOMIC PHYSICS

MODERN PHYSICS - PART 2
FORMULAE
PHOTOELECTRIC EFFECT

FREE
PDF
NOTES

ZENER DIODE

Semiconductor -1



CONCEPT
PYQs


JEE MAIN

by Mohit Goenka, IIT Kharagpur



TRANSISTORS JEE MAIN

Semiconductor -2

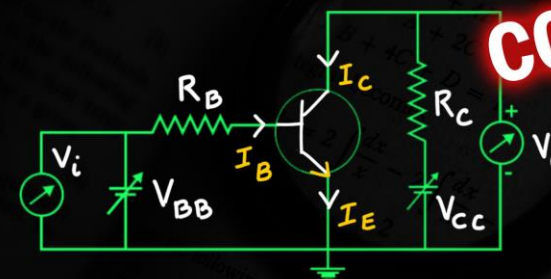

CONCEPT
PYQs

by Mohit Goenka, IIT Kharagpur



...MANY MORE




Eduniti for Physics

TOPICS COVERED


1. Analog and Digital Signal
2. Logic Gates (Types)
3. NOT Gate
4. AND Gate
5. OR Gate
6. Rules of Boolean Algebra & De Morgan's Theorem
7. NAND Gate
8. NOR Gate
9. Exclusive Gates (XOR & XNOR)
10. **PYQs** (Build your understanding)



1. ANALOG & DIGITAL SIGNAL

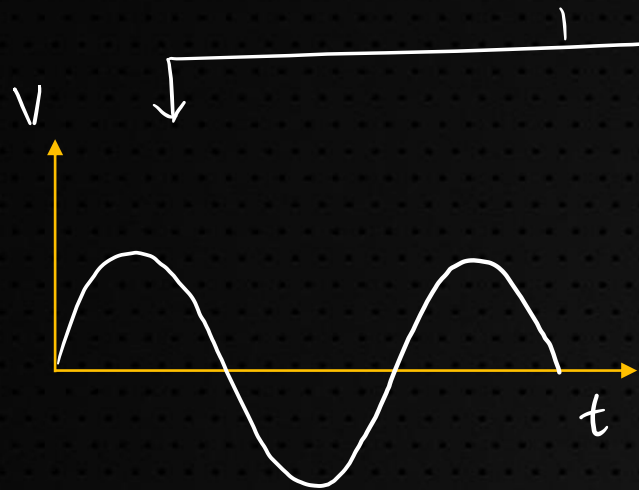

ANALOG SIGNAL

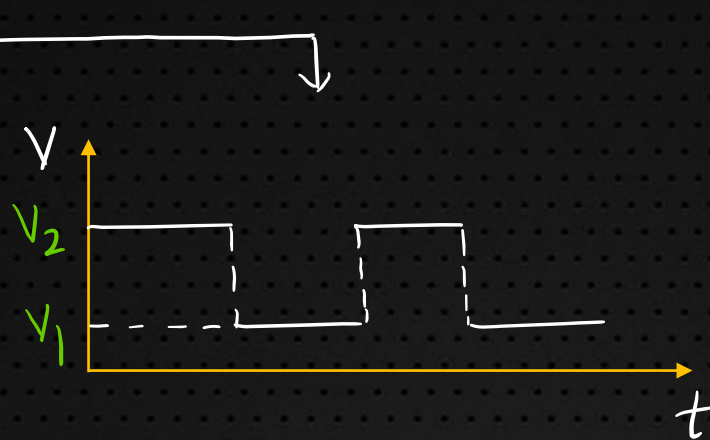

DIGITAL SIGNAL

↳ It has two states


(1.) High $\rightarrow 1$

(2.) Low $\rightarrow 0$


Logic gates are integral part of Digital Electronics

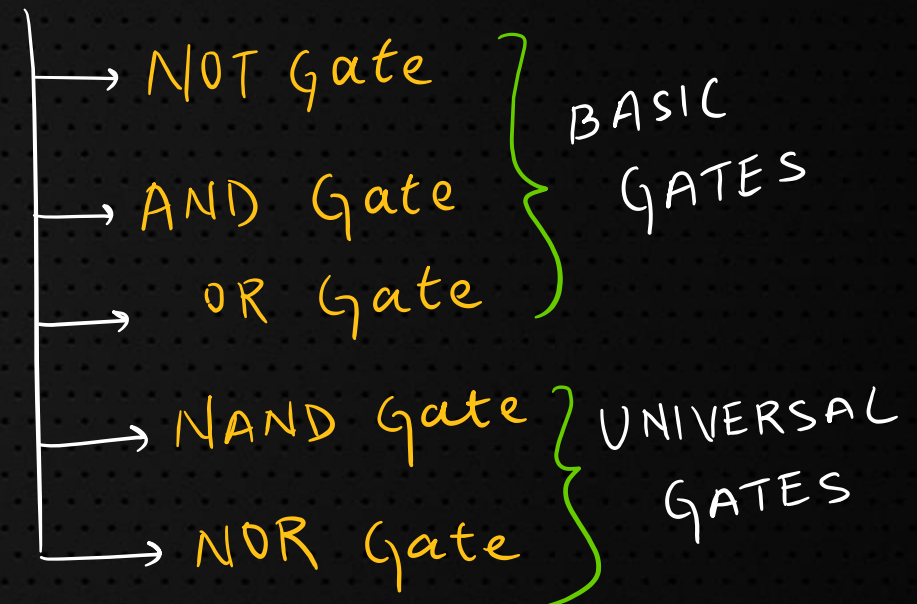2. LOGIC GATES

↳ Electrical circuits using logical relation between input and output voltages.



3. NOT GATE (Inversion Gate)

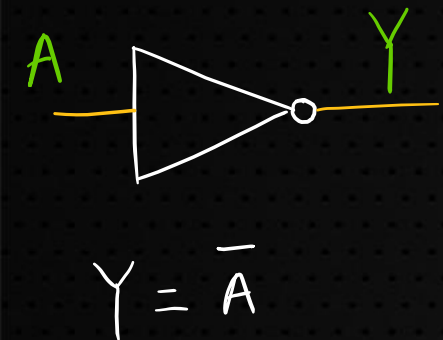

TRUTH TABLE

A	$Y = \bar{A}$
1	0
0	1

Truth Table : Relation between Input and Output.


4. AND GATE

→ output high (1), if both input is high (1)
 → output low (0), if either input is Low (0)



TRUTH TABLE

A	B	$Y = A \cdot B$
1	0	0
0	1	0
1	1	1
0	0	0

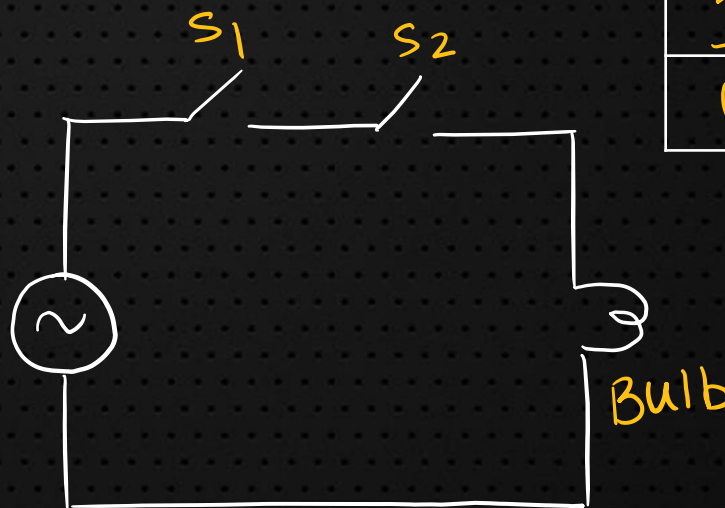

⇒ switch close : 1
 switch open : 0
 Bulb Glow = 1
 else = 0



5. OR GATE

- ↳ Output high (1), if either input is high (1)
- ↳ Output Low (0), if both input Low (0)



TRUTH TABLE

A	B	$Y = A + B$
1	0	1
0	1	1
1	1	1
0	0	0



6. RULES OF BOOLEAN ALGEBRA & DE MORGAN'S THEOREM

(a) $A + 0 = A$

(b) $A + A = A$

(c) $A \cdot A = A$

(d) $A \cdot \bar{A} = 0$

(e) $\bar{\bar{A}} = A$


DE MORGAN'S THEOREM

$$\overline{A \cdot B} = \bar{A} + \bar{B} \quad \overline{A + B} = \bar{A} \cdot \bar{B}$$

↳ Boolean Expressions



7. NAND GATE (AND + NOT)


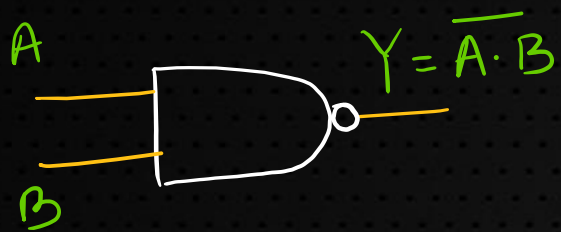


Inverts the AND gate output.

TRUTH TABLE

A	B	$Y = \overline{A \cdot B}$
1	0	1
0	1	1
1	1	0
0	0	1


NAND GATE (UNIVERSAL GATE)

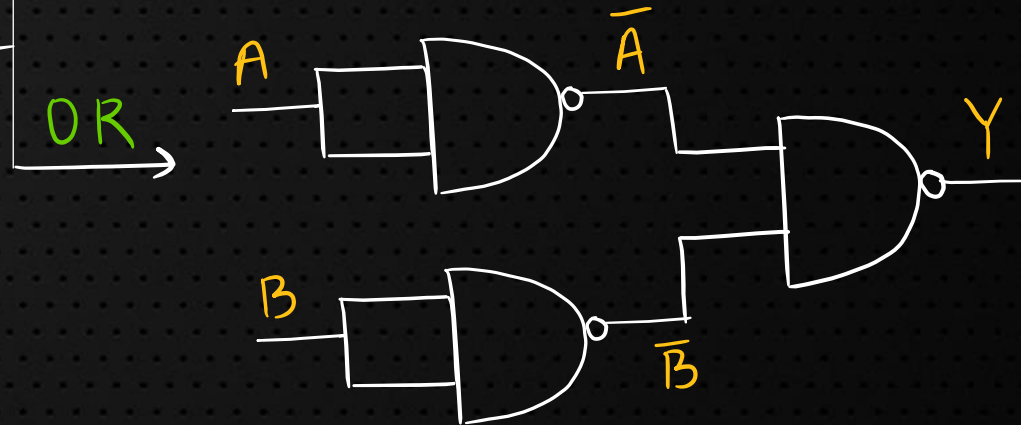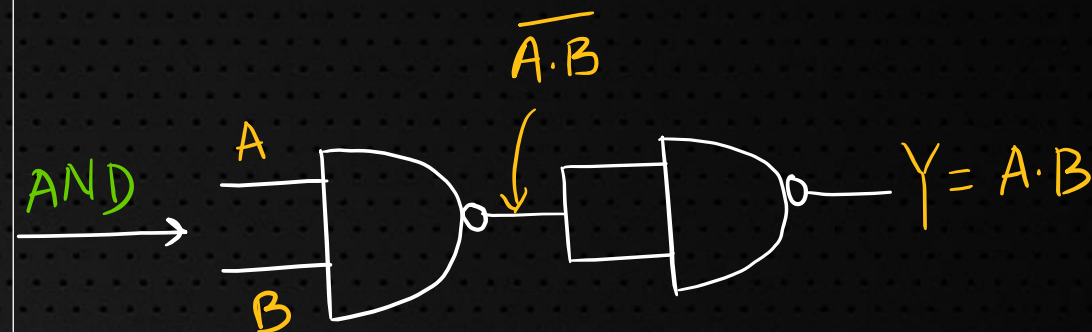

$Y = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A}} + \overline{\overline{B}} = \boxed{A + B}$



8. NOR GATE (OR + NOT)



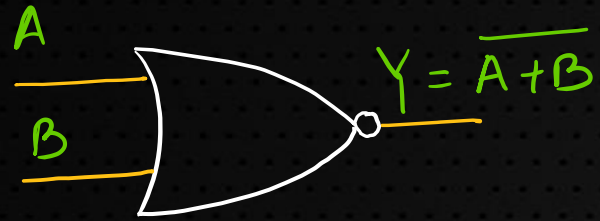


Inverts the AND gate output.

TRUTH TABLE

A	B	$Y = \overline{A+B}$
1	0	0
0	1	0
1	1	0
0	0	1


NOR GATE
(UNIVERSAL GATE)

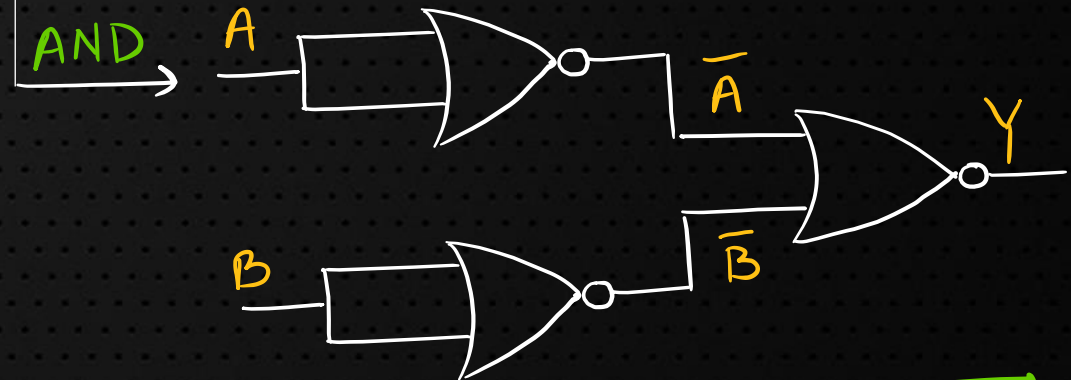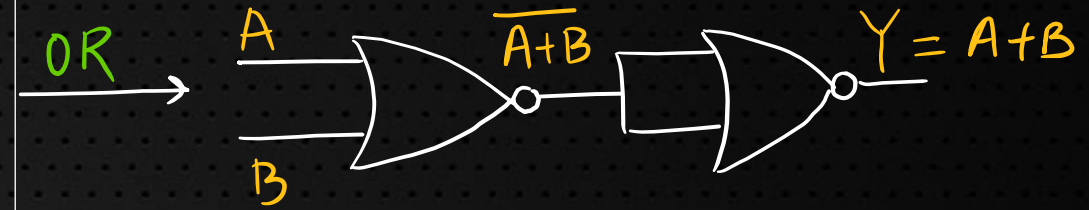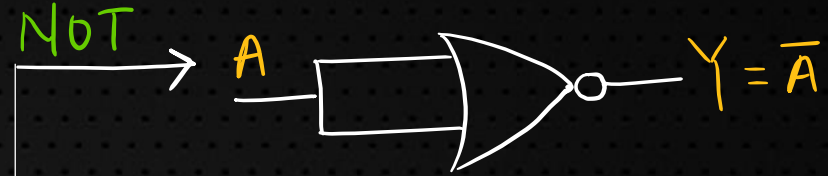

$Y = \overline{A+B} = \overline{\overline{A} \cdot \overline{B}} = \boxed{A \cdot B}$





9. EXCLUSIVE GATES

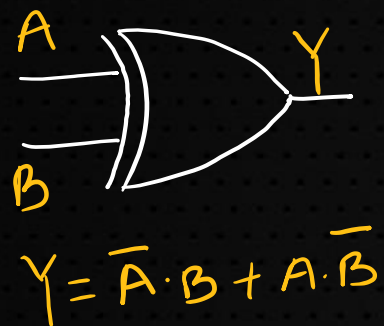

XOR (EXCLUSIVE OR GATE)

A	B	Y
1	0	1
0	1	1
1	1	0
0	0	0

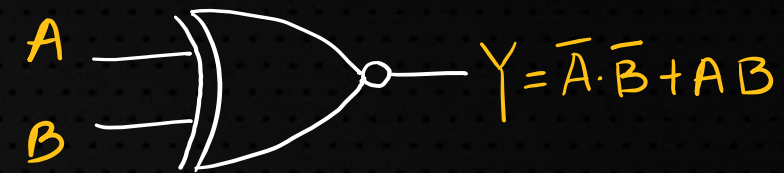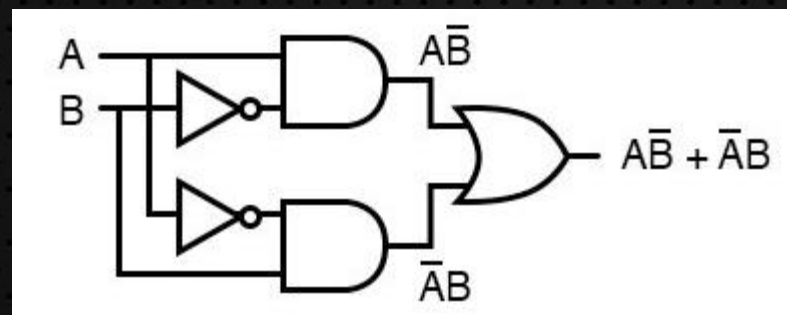

XNOR (EXCLUSIVE NOR GATE)

A	B	Y
1	0	0
0	1	0
1	1	1
0	0	1



Physics

Semiconductors Questions

JEE MAIN 2020

12 Questions

Mohit Goenka
IIT Kharagpur



LINK IN VIDEO
DESCRIPTION
BOX.

SEMICONDUCTORS

JEE MAIN 2021

July Attempt Solution

Mohit Goenka | IIT Kharagpur



Physics

SEMICONDUCTOR Questions

JEE 2021

Feb Attempt

Mohit Goenka
IIT Kharagpur

