

JEE MAIN

CAPACITORS

FORMULAE

Now that's how you REVISE

-Mohit Goenka, IIT Kharagpur

List of Content on Eduniti YouTube Channel:

1. PYQs Video Solution Topic Wise:
 - (a) JEE Main 2018/2020/2021 Feb & March
2. Rank Booster Problems for JEE Main
3. Part Test Series for JEE Main
4. JEE Advanced Problem Solving Series
5. Short Concept Videos
6. Tips and Tricks Videos
7. JEE Advanced PYQs

.....and many more to come



EDUNITI




Eduniti for Physics

CAPACITORS


1. Spherical and Cylindrical Capacitors
2. Parallel Plate capacitors
3. Charge, Energy Stored, Work done by Battery, Heat
4. Force Between Plates
5. Series / Parallel
6. Alternative figure for plate arrangement
7. Wheatstone bridge (Balanced & Unbalanced)
8. Charge Sharing & Heat generated
9. Dielectric in Electric Field (Induced Charge)
10. Dielectric Slab in Capacitor
11. Effect of slab insertion in a capacitor (at Const. V and Q)
12. Capacitance for Multiple Dielectric Medium
13. Capacitance for Variable K
14. Capacitance for variable dimensions
15. RC – Charging and Discharging



1. CAPACITANCE (unit: Farad)

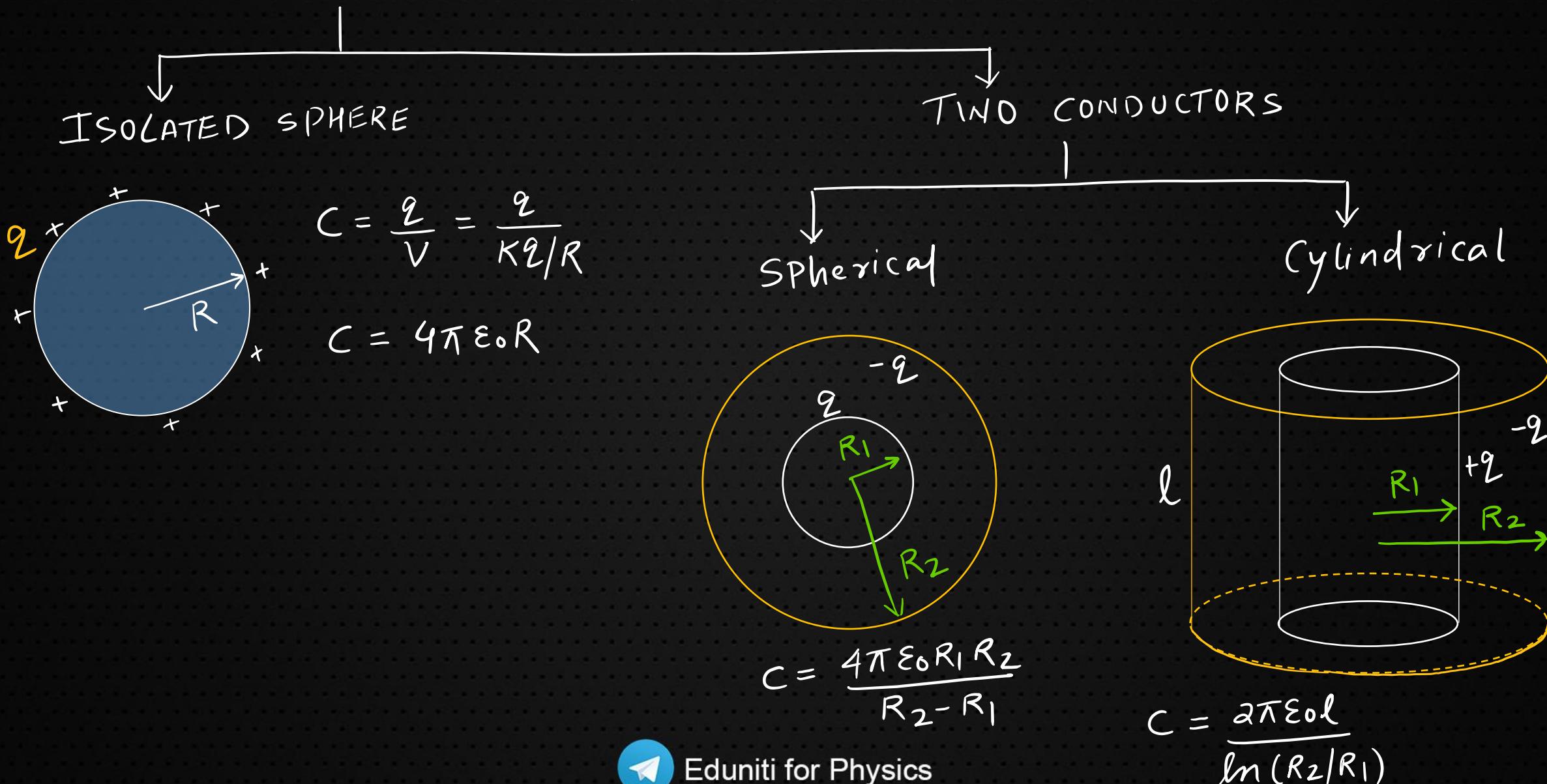

2. PARALLEL PLATE CAPACITOR


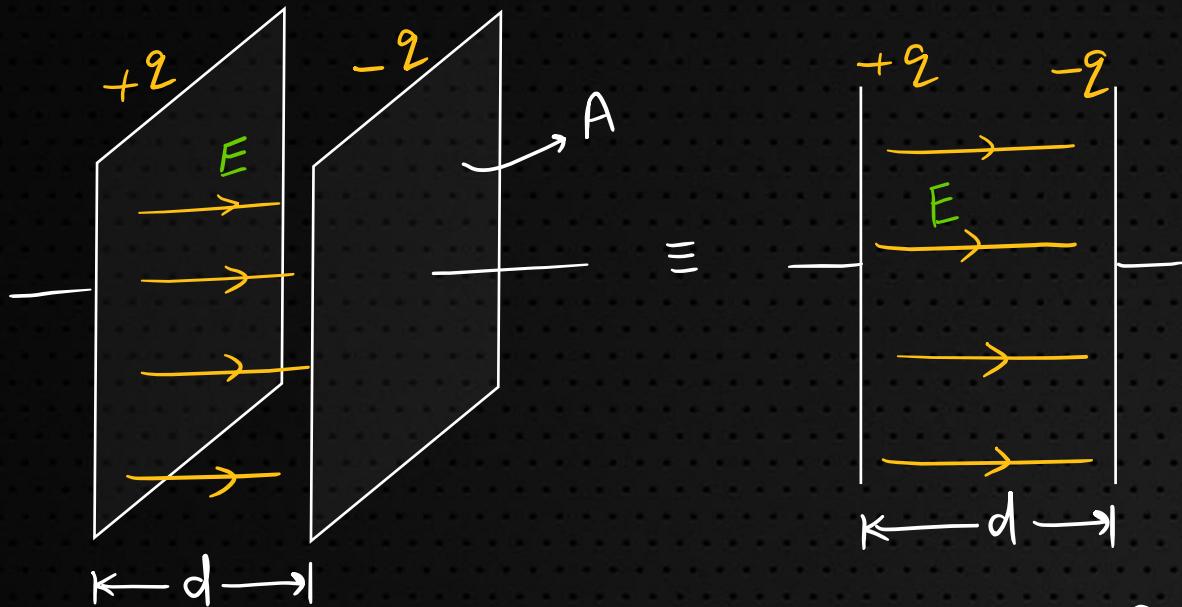


$$C = q/v = q/Ed$$

$$(E = \frac{\sigma}{\epsilon_0} = \frac{q}{A\epsilon_0})$$

$$\Rightarrow C = \frac{A\epsilon_0}{d}$$

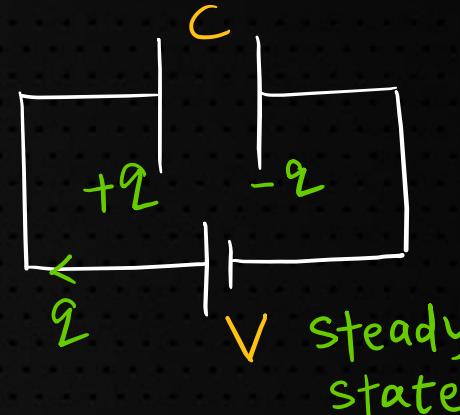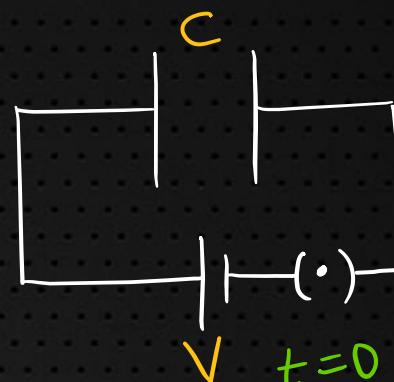3. CHARGE / ENERGY STORED W_{battery} / HEAT DISSIPATION



$$(i) q = CV$$

$$(ii) W_b = q_{\text{flown}} \times V = CV^2$$

$$(iii) V = \frac{1}{2}CV^2 \quad \{ q^2/2C \}$$

$$(iv) \text{Heat Dissipated} \\ = W_b - \Delta U \\ = CV^2 - \frac{1}{2}CV^2 = \frac{1}{2}CV^2$$



4. FORCE BETWEEN PLATES




$$F = q \times E_{-q} = q \times \frac{q}{2A\epsilon_0}$$

$$\Rightarrow F = q^2 / 2A\epsilon_0$$

x = spring elongation


ex:

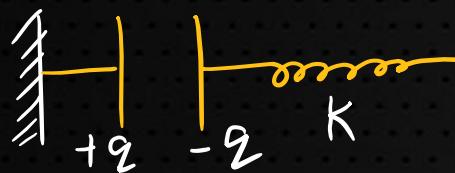

$$\therefore Kx = \frac{q^2}{2A\epsilon_0}$$


- NOTE: (a) n identical capacitor in series, $C_{eq} = C/n$
- (b) If in Parallel, $C_{eq} = nC$

5. COMBINATION OF CAPACITOR

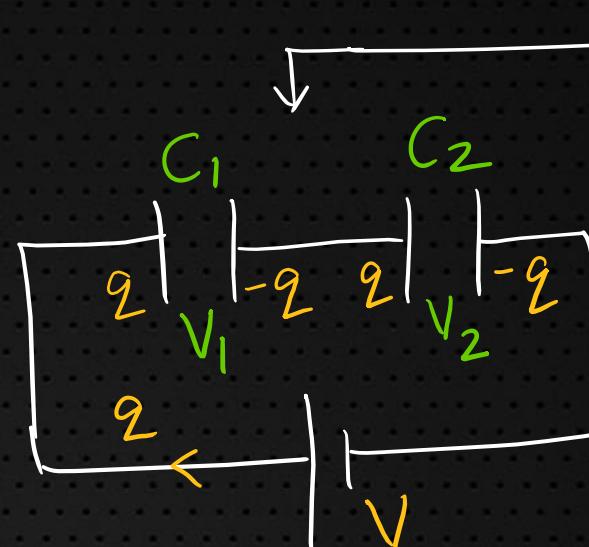

$$(i) C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$(ii) q = C_{eq}V$$

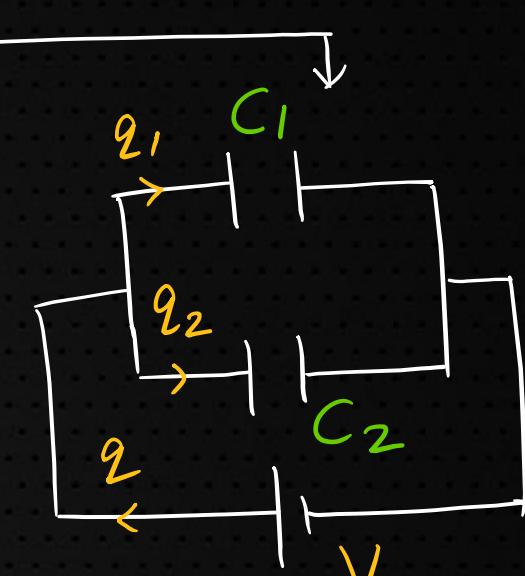

$$C_{eq} = C_1 + C_2$$

$$q_1 = C_1 V, q_2 = C_2 V$$




Alternatively:




Identical plates


$$C = A \epsilon_0 / d$$

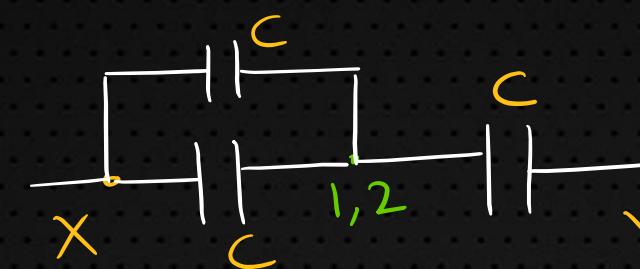

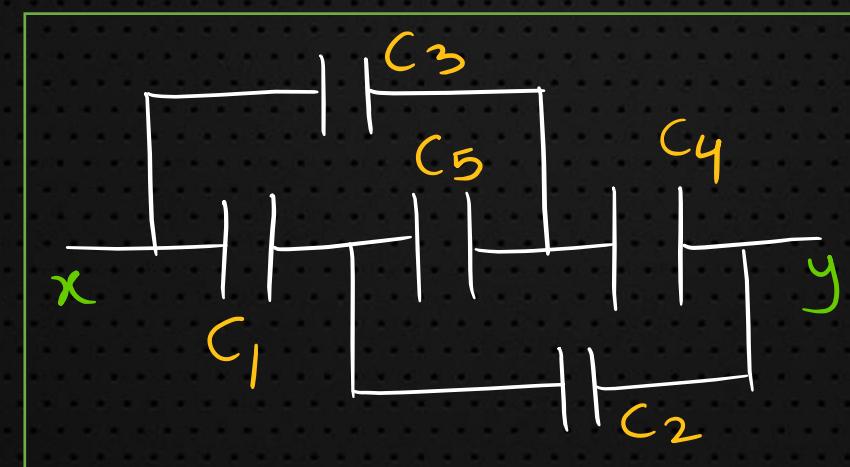
$$C_{eq} = \frac{2C}{3} = \frac{2A\epsilon_0}{3d}$$



6. WHEATSTONE BRIDGE (BALANCED)

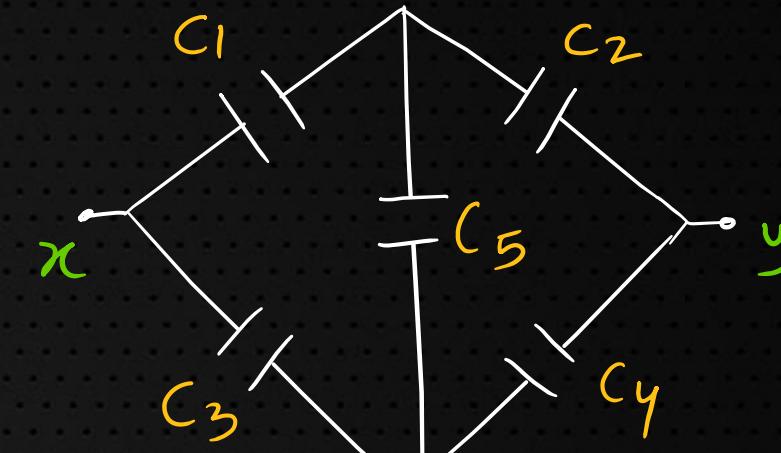

If $C_1 C_4 = C_2 C_3$

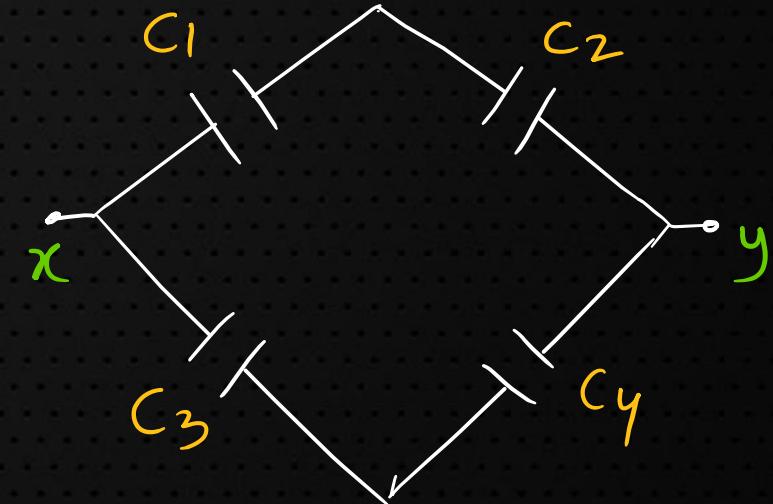

7. TECHNIQUE FOR UNBALANCED WHEATSTONE BRIDGE ($C_1C_4 \neq C_2C_3$) (Point Potential + Junction Rule)

At x : $C_1(x-V) + C_5(x-y) + C_2(x-0) = 0$ $\quad \text{--- (1)}$


At y : $C_3(y-V) + C_5(y-x) + C_4(y-0) = 0$ $\quad \text{--- (2)}$

(a) solve (1) and (2) to find x and y .

(b) Then we can find q_1, q_2, q_3, q_4 and q_5

(c) $q = q_1 + q_3$


(d) $C_{eq} = \frac{q}{V}$

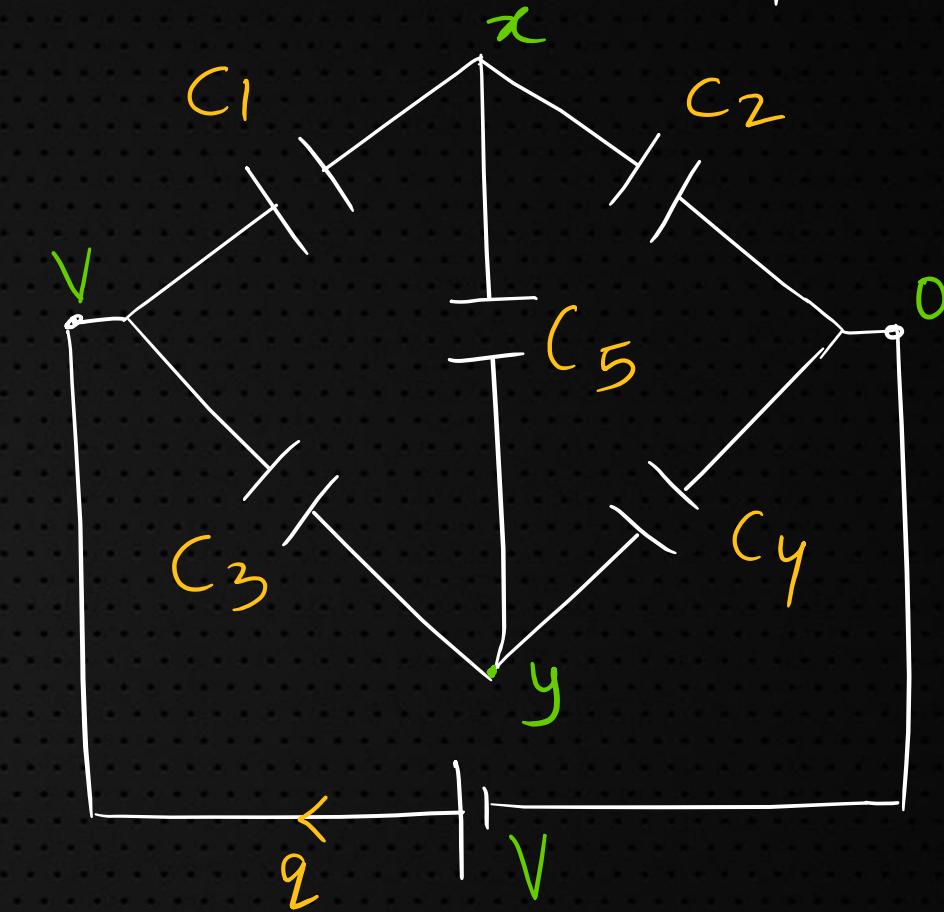

#NOTE : This method can be used to solve any kind of circuit.

8. CHARGE SHARING AND HEAT GENERATED

(a) CONNECTED SAME POLARITY

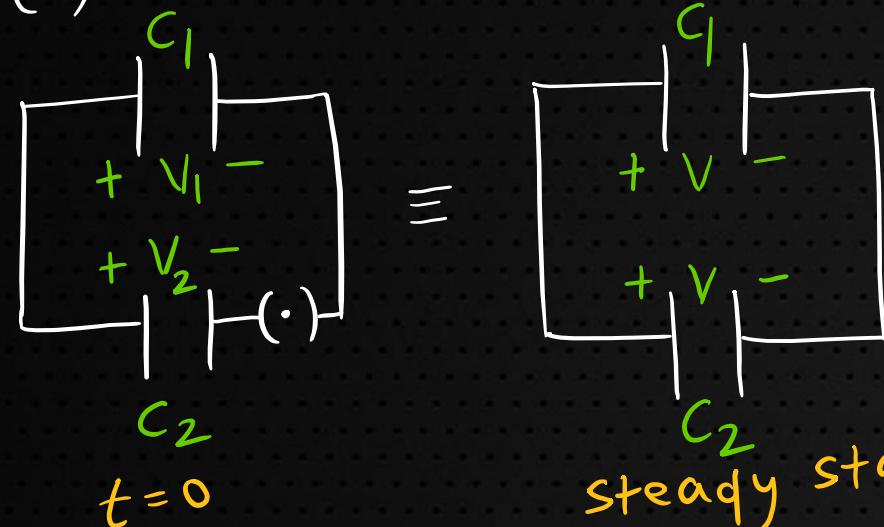


$$(i) V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \quad (ii) H = \frac{C_1 C_2}{2(C_1 + C_2)} (V_1 - V_2)^2$$

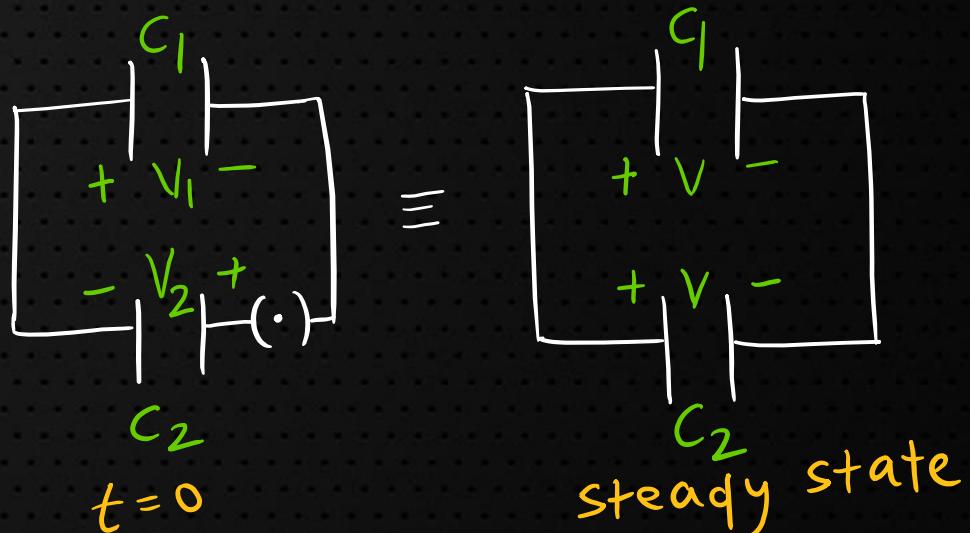(b) CONNECTED OPPOSITE POLARITY
steady state


$$(i) V = \frac{C_1 V_1 - C_2 V_2}{C_1 + C_2}$$

$$(ii) H = \frac{C_1 C_2}{2(C_1 + C_2)} (V_1 + V_2)^2$$



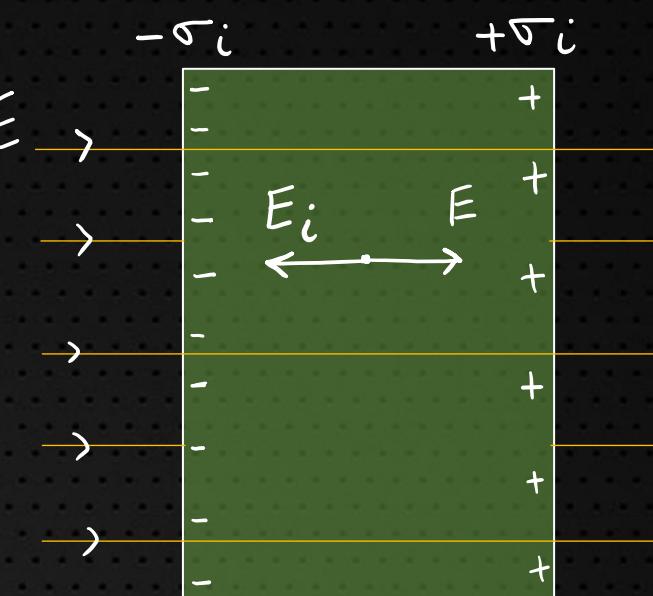9. DIELECTRIC IN EXTERNAL ELECTRIC FIELD

- Insulators (gets Polarized in E)
- Dielectric constant (K or ϵ_r)
 - ↳ for air/vacuum $K=1$
 - for metal $K \rightarrow \infty$




$$E_{\text{net}} = E - E_i$$

$$\Rightarrow \frac{E}{K} = E - \frac{\sigma_i}{\epsilon_0}$$

$$\Rightarrow \sigma_i = \epsilon_0 E \left(1 - \frac{1}{K}\right)$$

Induced charge density, $\sigma_i = \frac{Q_i}{A}$

10. SLAB IN CAPACITOR

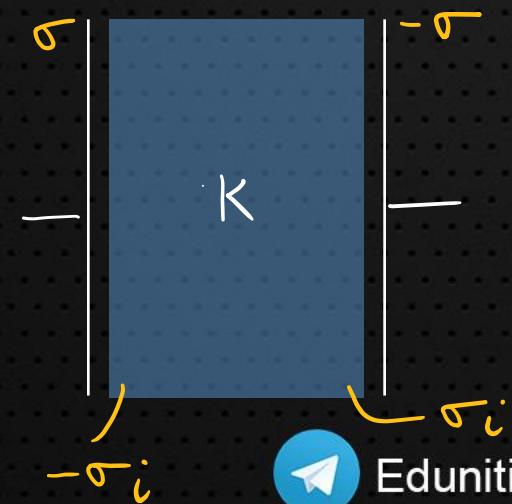

$$(i) C = KA\epsilon_0/d$$


$$(ii) \sigma_i = \sigma \left(1 - \frac{1}{K}\right)$$

$$Q_i = Q \left(1 - \frac{1}{K}\right)$$



11. EFFECT OF INSERTING DIELECTRIC IN CAPACITOR

(a) At constant V (Battery connected)

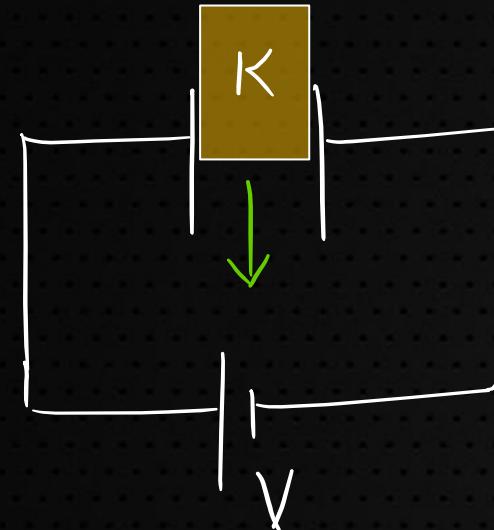


- (i) $C \rightarrow KC$ ($C \uparrow$)
- (ii) $Q \rightarrow KQ$ ($Q \uparrow$)
- (iii) V is const.
- (iv) E is const. ($E = \frac{V}{d}$)

$$(V) V \rightarrow KV \quad (V \uparrow)$$

$$\left(V = \frac{1}{2} CV^2 \right)$$

$$V = \frac{Q^2}{2C}$$

(b) At constant charge (Battery removed)

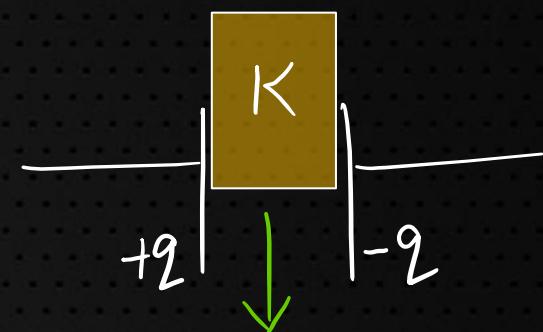


- (i) Q is const.
- (ii) $C \rightarrow KC$ ($C \uparrow$)
- (iii) $V \rightarrow \frac{V}{K}$ ($V \downarrow$)
- (iv) $E \rightarrow E/K$ ($E \downarrow$)
- (v) $V \rightarrow V/K$ ($V \downarrow$)

$$(V = Q/C)$$




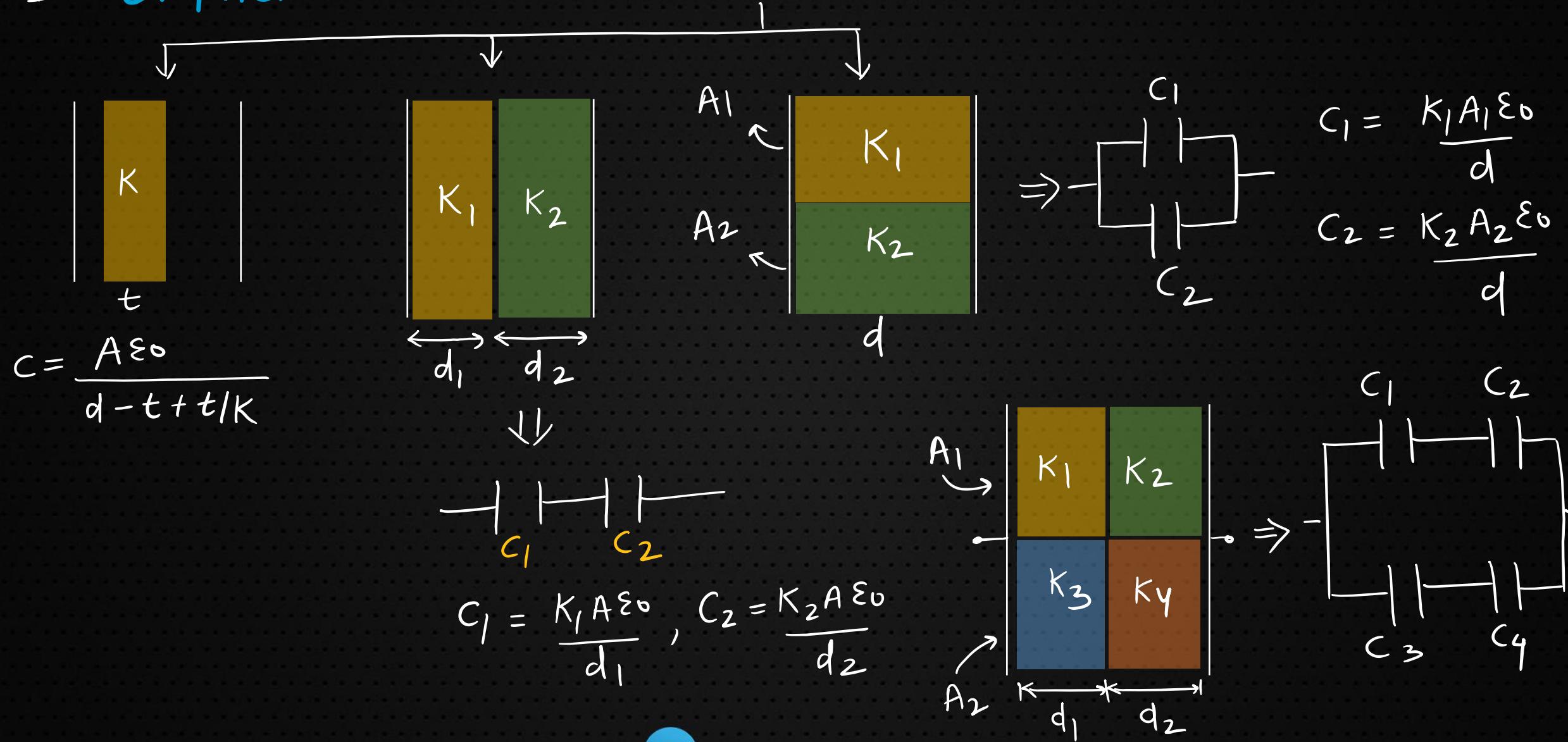12. CAPACITANCE FOR MULTIPLE DIELECTRIC MEDIUM




13. CAPACITANCE WITH VARIABLE K

(a)

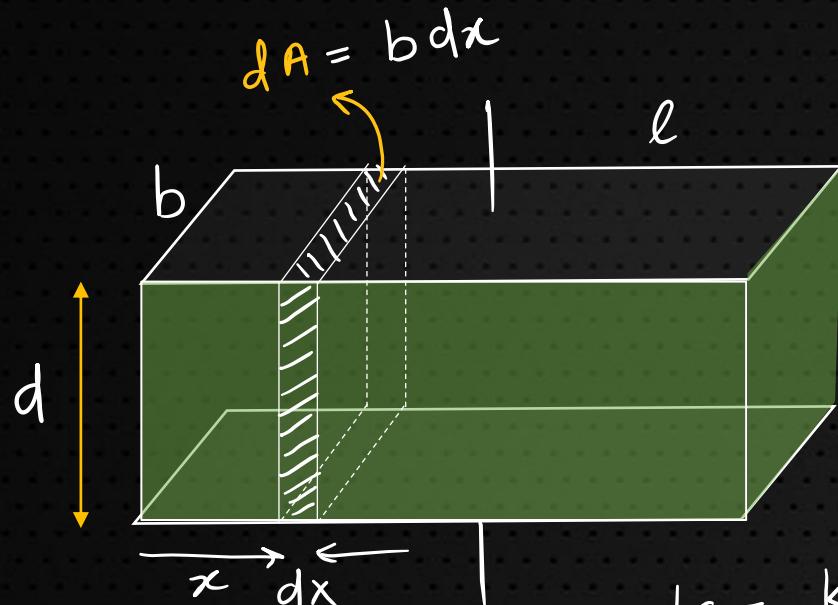

(b)

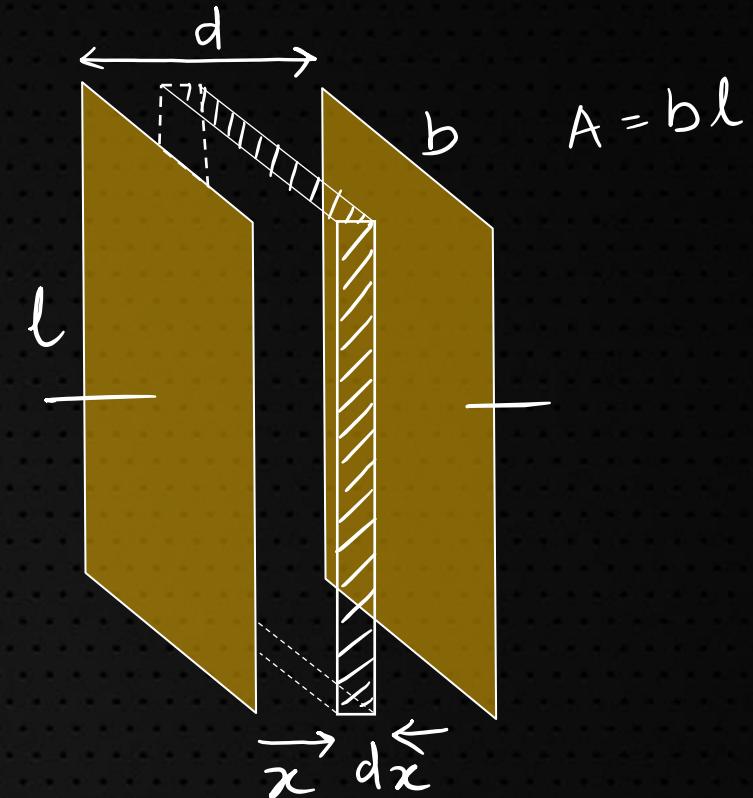

$$dC = \frac{K(x) b dx \epsilon_0}{d}$$


$$\Rightarrow C = \frac{b \epsilon_0}{d} \int_0^l K(x) dx$$

$$dC = \frac{K(x) A \epsilon_0}{dx}$$


$$\Rightarrow \frac{1}{C} = \int \frac{1}{dC} = \frac{1}{A \epsilon_0} \int_0^d \frac{dx}{K(x)}$$



14. CAPACITANCE WITH VARIABLE DIMENSIONS

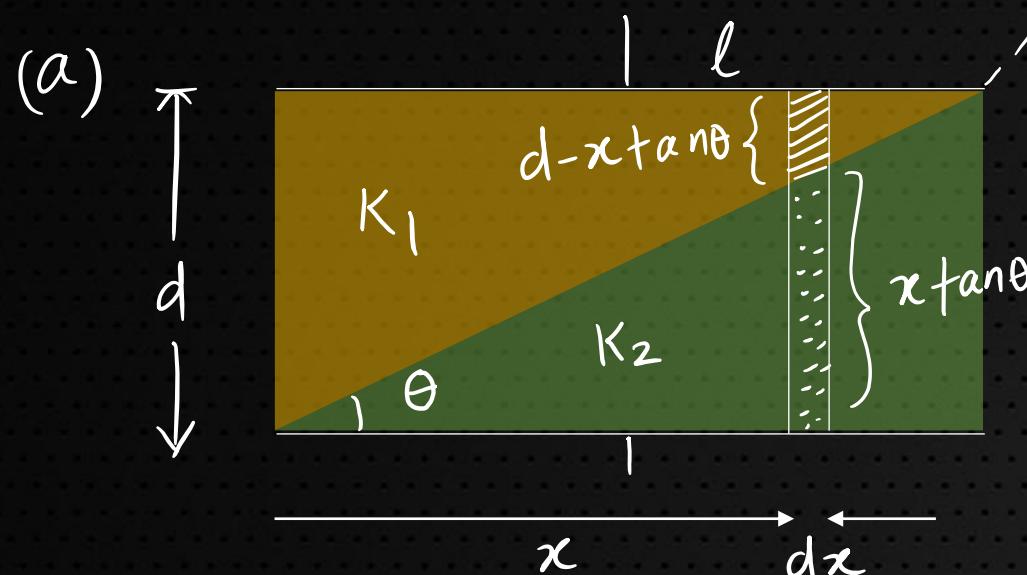

(b)

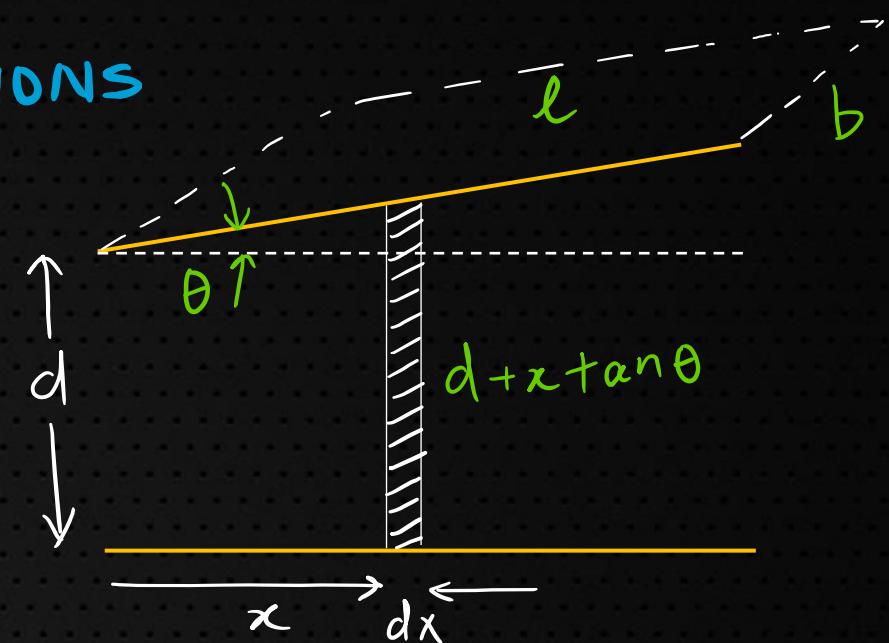

$$dC_1 = \frac{K_1 b dx \epsilon_0}{d - x \tan \theta}, \quad dC_2 = \frac{K_2 b dx}{x \tan \theta}$$

$$dC_{eq} = \frac{dC_1 \times dC_2}{dC_1 + dC_2}$$

$$C_{eq} = \int_0^l dC_{eq}$$

$$dC = \frac{bdx \epsilon_0}{d + x \tan \theta}$$

$$\therefore C = b \epsilon_0 \int_0^l \frac{dx}{d + x \tan \theta}$$



15. RC, CHARGING AND DISCHARGING



At $t=0, q=0$


$$\text{At } t=t, q = q_0 (1 - e^{-t/RC}) \quad q_0 = CV$$

$RC = \tau$, time const.

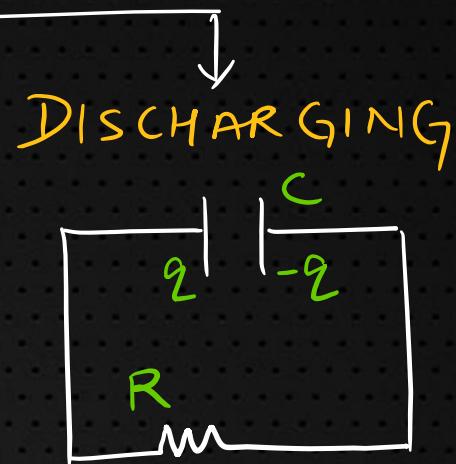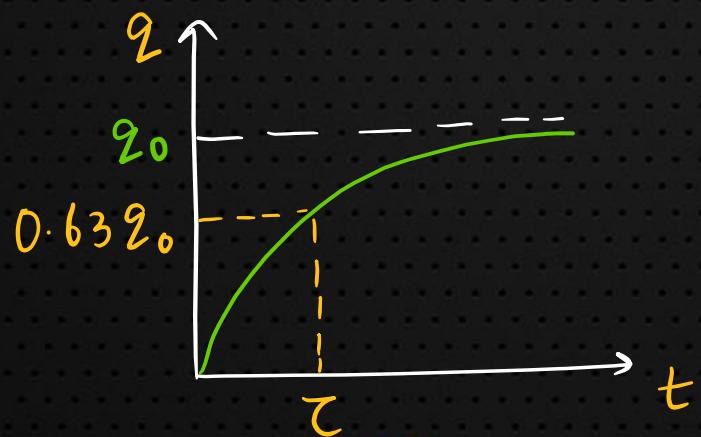

at $t=0, q=q_0$

$$\text{at } t=t, q = q_0 e^{-t/RC}$$

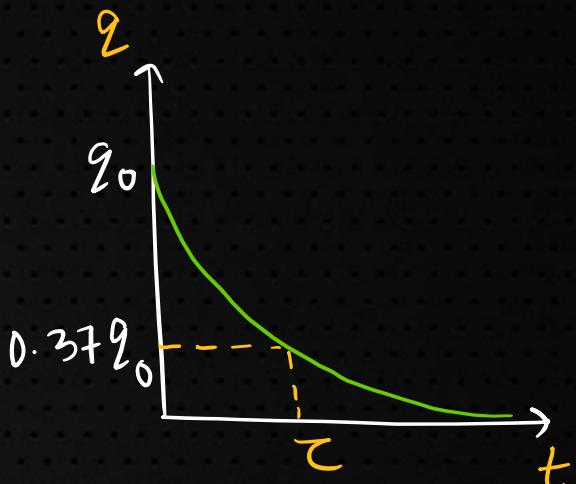

NOTE:

- (1.) At $t=0$, capacitor behaves as conducting wire
- (2) At steady state it acts as open circuit.

