



**JEE 2022**

**LR CIRCUIT**

**GROWTH & DECAY**

**MOHIT SIR-IIT KGP**



## TOPICS TO BE DISCUSSED



1. Growth of Current
2. Decay of Current
3. 4 Questions (PYQs)



Eduniti for Physics

JOIN

# 1. Growth of Current

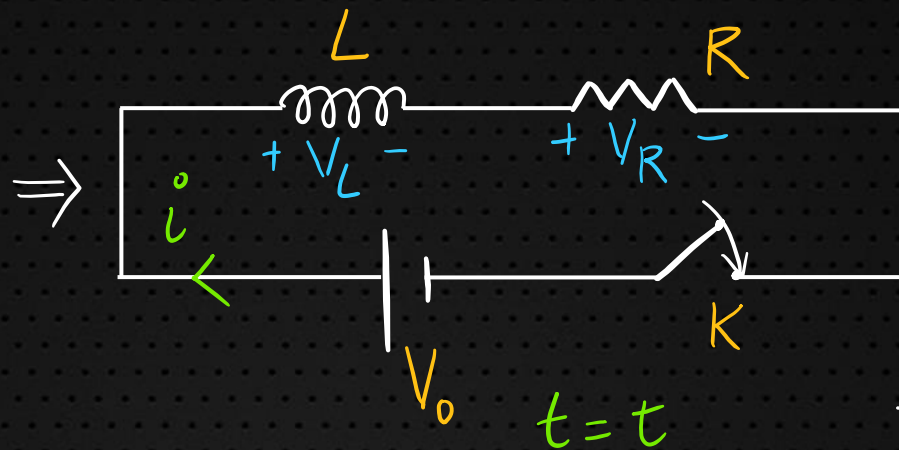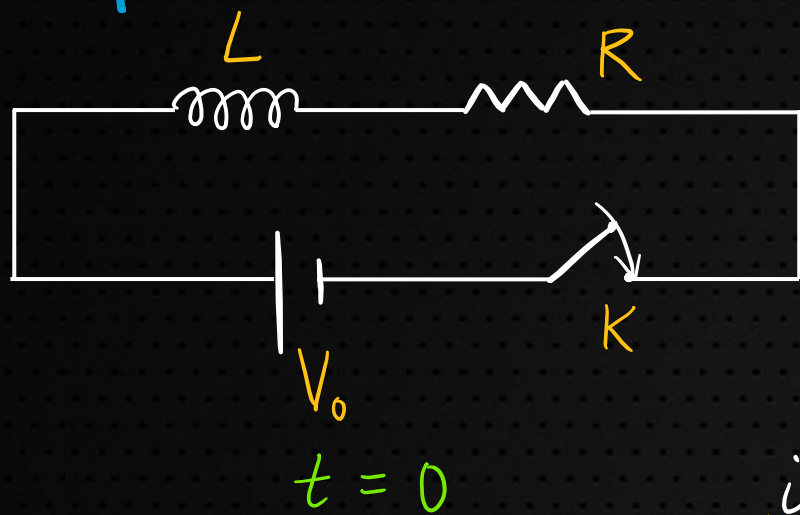

$$V_L + V_R = V_0$$


$$\Rightarrow L \frac{di}{dt} + iR = V_0$$

$$\Rightarrow \int_0^i \frac{di}{V_0 - iR} = \int_0^t \frac{dt}{L}$$

$$\Rightarrow i = \frac{V_0}{R} \left( 1 - e^{-Rt/L} \right)$$

(i)  $\tau = L/R$

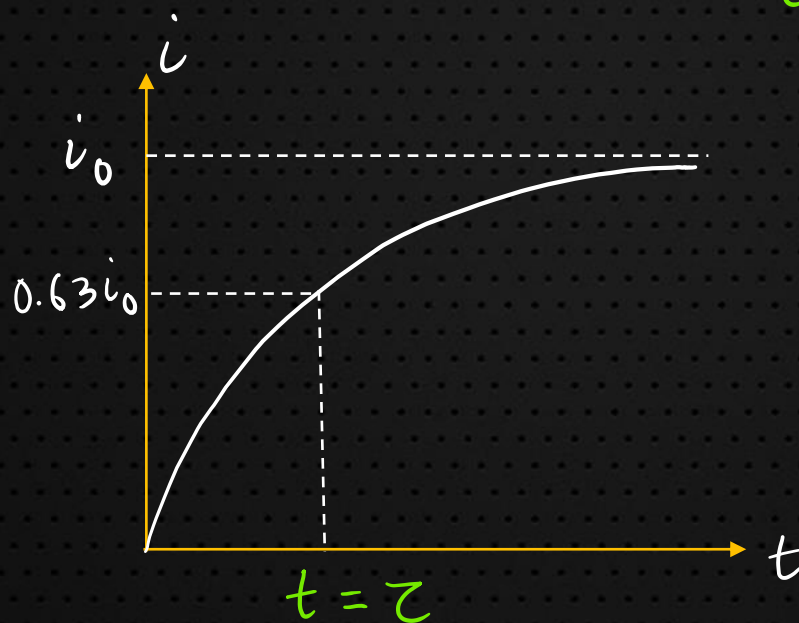(ii)  $i_0 = \frac{V_0}{R}$  at  $t \rightarrow \infty$





... Continued

Key points

$$i = i_0 (1 - e^{-Rt/L})$$


→ At  $t=0$ ,  $i=0$  (inductor behaves as open circuit)



→ At  $t \rightarrow \infty$ ,  $i = i_0 = \frac{V_0}{R}$  (steady state, inductor behaves as conducting wire)



## 2. Decay of current

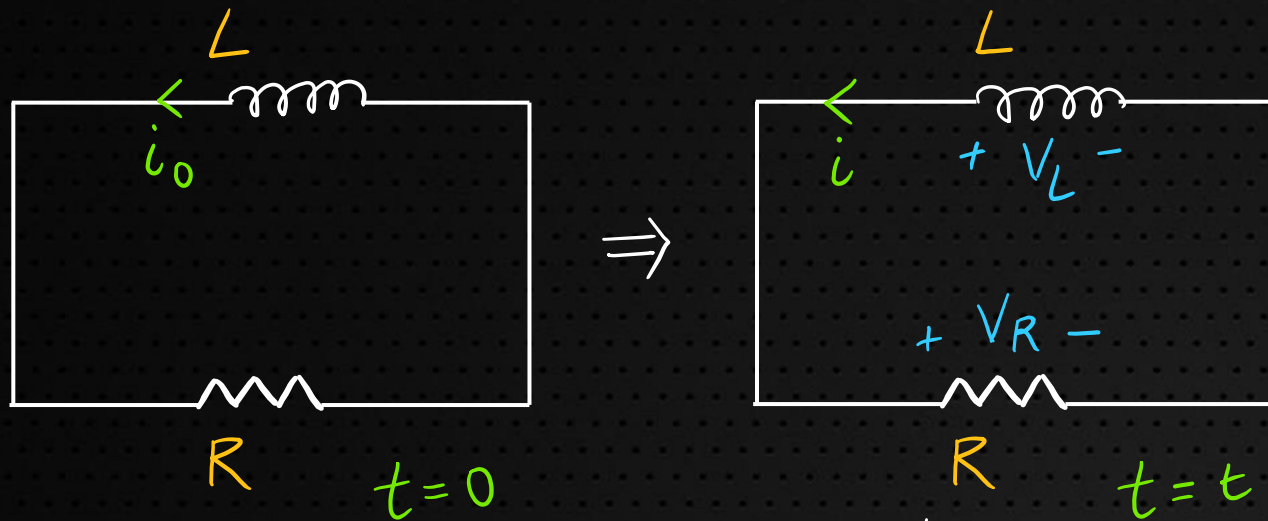


$$V_L = V_R \Rightarrow -L \frac{di}{dt} = iR$$

$$\Rightarrow \int_{i_0}^i \frac{di}{i} = \int_0^t -\frac{R}{L} dt$$

$$\Rightarrow i = i_0 e^{-Rt/L}$$

$$\hookrightarrow \tau = L/R$$

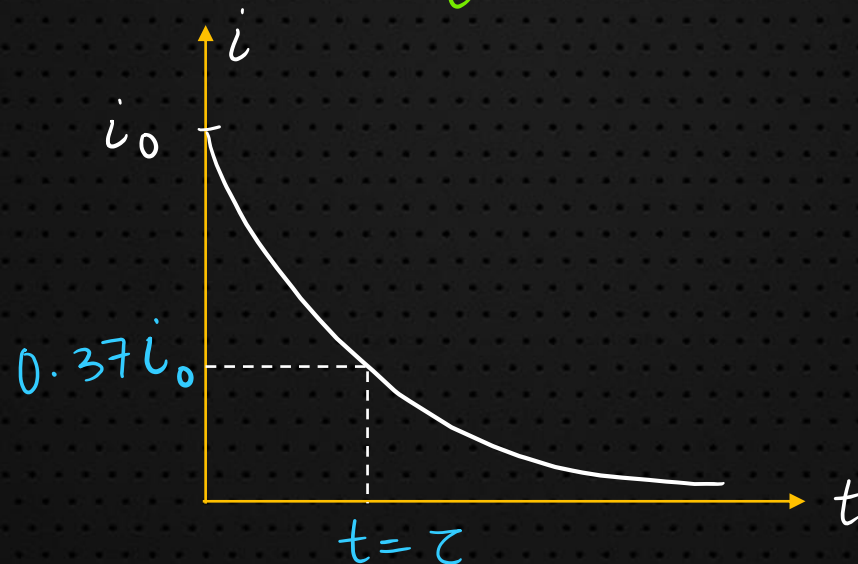

Q1.

A coil of self inductance  $10\text{ mH}$  and resistance  $0.1\ \Omega$  is connected through a switch to a battery of internal resistance  $0.9\ \Omega$ . After the switch is closed, the time taken for the current to attain 80% of the saturation value is [Take,  $\ln 5 = 1.6$ ]

(Main 2019, 10 April II)

(a)  $0.002\text{ s}$

(b)  $0.324\text{ s}$

(c)  $0.103\text{ s}$

(d)  $0.016\text{ s}$





Q1.

A coil of self inductance 10 mH and resistance 0.1  $\Omega$  is connected through a switch to a battery of internal resistance 0.9  $\Omega$ . After the switch is closed, the time taken for the current to attain 80% of the saturation value is [Take,  $\ln 5 = 1.6$ ]  
(Main 2019, 10 April II)

- (a) 0.002 s  
(c) 0.103 s

- (b) 0.324 s  
(d) 0.016 s

Sol<sup>n</sup>:  $i = i_0 \left( 1 - e^{-\frac{Rt}{L}} \right)$

$$R = 0.1 + 0.9 = 1 \Omega$$

$$L = 10 \text{ mH} = 10^{-2} \text{ H}$$

$$i = 0.8 i_0$$

$$\Rightarrow 0.8 i_0 = i_0 \left( 1 - e^{-\frac{t}{10^{-2}}} \right)$$


$$\Rightarrow 5^{-1} = e^{-100t} \Rightarrow \ln 5 = 100t$$

$$\therefore t = \frac{1.6}{100} = \boxed{0.016 \text{ s}}$$



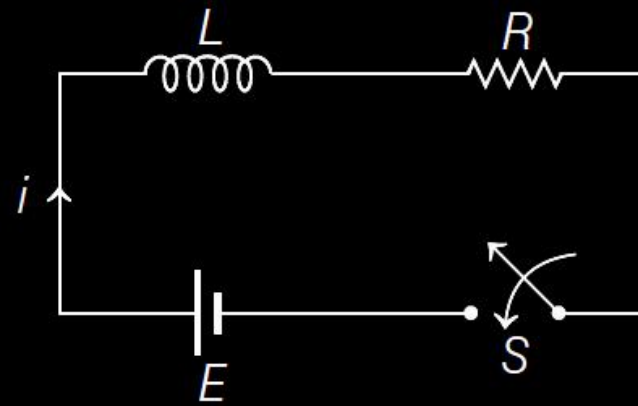Q2.

Consider the  $L$ - $R$  circuit shown in the figure. If the switch  $S$  is closed at  $t = 0$ , then the amount of charge that passes through the battery between  $t = 0$  and  $t = \frac{L}{R}$  is (Main 2019, 12 April II)



- (a)  $\frac{2.7EL}{R^2}$       (b)  $\frac{EL}{2.7R^2}$       (c)  $\frac{7.3EL}{R^2}$       (d)  $\frac{EL}{7.3R^2}$






Sol<sup>n</sup>:  $i = i_0 (1 - e^{-Rt/L})$  Q2.

$$\Rightarrow \frac{dq}{dt} = \frac{E}{R} (1 - e^{-Rt/L})$$

$$\Rightarrow \int_0^q dq = \frac{E}{R} \int_0^{L/R} (1 - e^{-Rt/L}) dt$$

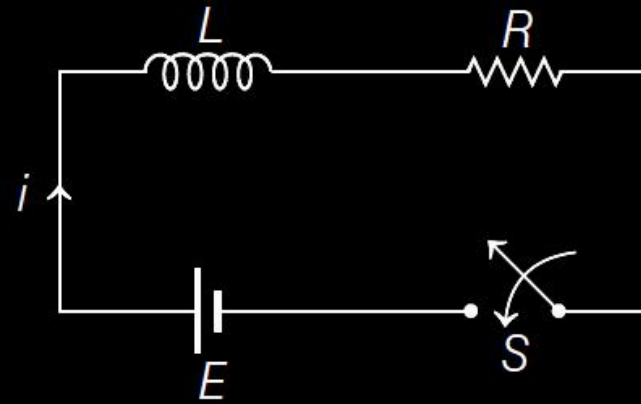Consider the  $L$ - $R$  circuit shown in the figure. If the switch  $S$  is closed at  $t = 0$ , then the amount of charge that passes through the battery between  $t = 0$  and  $t = \frac{L}{R}$  is (Main 2019, 12 April II)




- (a)  $\frac{2.7EL}{R^2}$  (b)  $\frac{EL}{2.7R^2}$  (c)  $\frac{7.3EL}{R^2}$  (d)  $\frac{EL}{7.3R^2}$

$$\Rightarrow q = \frac{E}{R} \left( t + \frac{L}{R} e^{-\frac{Rt}{L}} \right) \Big|_0^{L/R} \Rightarrow q = \frac{EL}{eR^2} = \boxed{\frac{EL}{2.7R^2}}$$



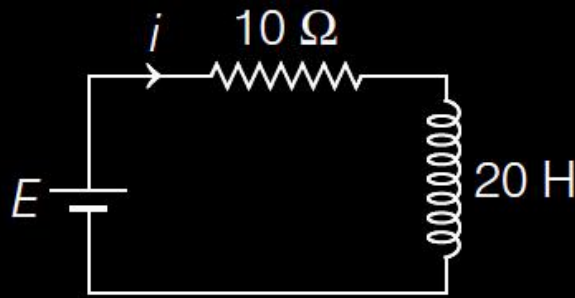Q3. A 20 H inductor coil is connected to a 10 ohm resistance in series as shown in figure. The time at which rate of dissipation of energy (Joule's heat) across resistance is equal to the rate at which magnetic energy is stored in the inductor, is




(Main 2019, 10 Jan I)

- (a)  $\frac{2}{\ln 2}$       (b)  $\frac{1}{2} \ln 2$       (c)  $2 \ln 2$       (d)  $\ln 2$





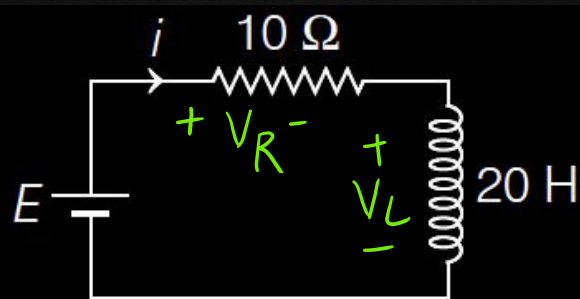Q3. A 20 H inductor coil is connected to a 10 ohm resistance in series as shown in figure. The time at which rate of dissipation of energy (Joule's heat) across resistance is equal to the rate at which magnetic energy is stored in the inductor, is



(Main 2019, 10 Jan I)

- (a)  $\frac{2}{\ln 2}$       (b)  $\frac{1}{2} \ln 2$       (c)  $2 \ln 2$       (d)  $\ln 2$

sol<sup>n</sup>:

$$P_R = P_L$$

$$\Rightarrow i V_R = i V_L \Rightarrow V_R = V_L$$

$$\therefore V_R = E/2$$

$$\Rightarrow i R = E/2 \Rightarrow i_0 (1 - e^{-\frac{Rt}{L}}) R = \frac{E}{2}$$

$$\Rightarrow \frac{E}{R} (1 - e^{-\frac{Rt}{L}}) R = \frac{E}{2}$$

$$\therefore e^{-\frac{Rt}{L}} = \frac{1}{2} \Rightarrow t = \frac{L}{R} \ln 2$$

$$= \boxed{2 \ln 2}$$






Q4.

An inductor ( $L = 0.03 \text{ H}$ ) and a resistor ( $R = 0.15 \text{ k}\Omega$ ) are connected in series to a battery of  $15\text{V}$  EMF in a circuit shown below. The key  $K_1$  has been kept closed for a long time. Then at  $t = 0$ ,  $K_1$  is opened and key  $K_2$  is closed simultaneously. At  $t = 1\text{ms}$ , the current in the circuit will be ( $e^5 \cong 150$ )

(2015 Main)

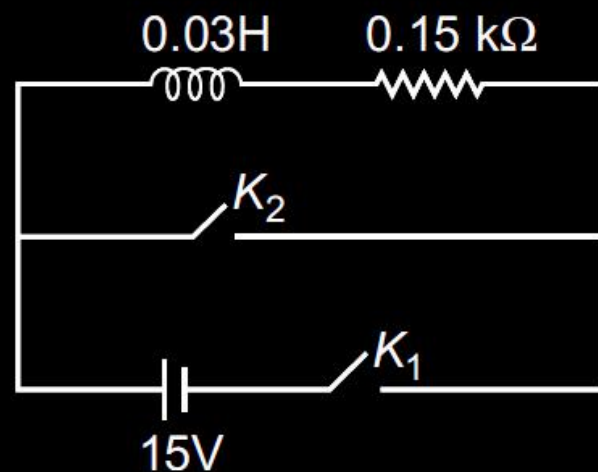

- (a) 100 mA    (b) 67 mA    (c) 0.67mA    (d) 6.7 mA



sol<sup>n</sup>:  $K_1$  closed Q4.  
 $\hookrightarrow i_0 = \frac{E}{R} = \frac{15}{150} = \frac{1}{10} \text{ A}$


$K_1$  open,  $K_2$  closed:

$i_0 = \frac{1}{10} \text{ A}$        $i = i_0 e^{-Rt/L}$   
 $\Rightarrow i = \frac{1}{10} e^{-\frac{150 \times 10^{-3}}{3 \times 10^{-2}}}$

$\therefore i = 0.1 \times e^{-5}$   
 $= 0.1 \times \frac{1}{e^5}$

$= 0.1 \times \frac{1}{150} \text{ A} \approx \boxed{0.67 \text{ mA}}$

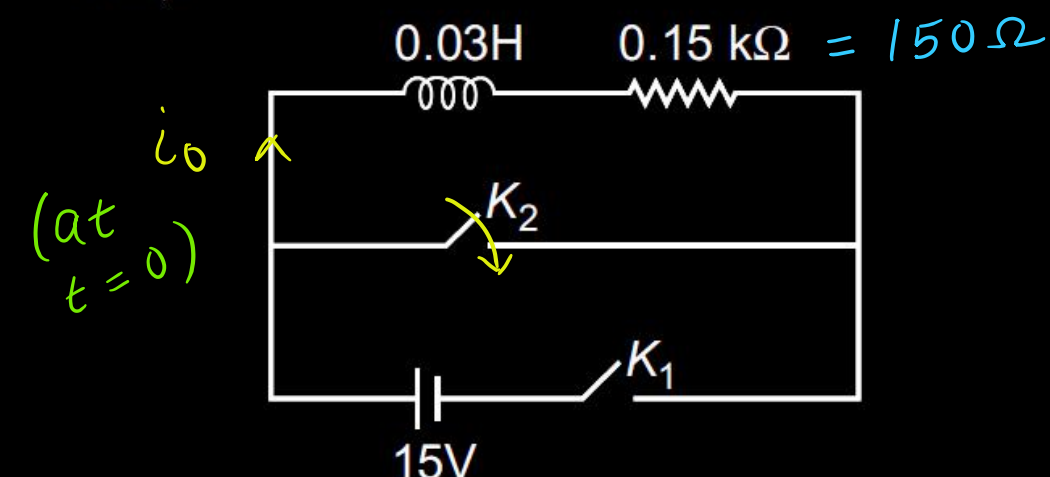An inductor ( $L = 0.03 \text{ H}$ ) and a resistor ( $R = 0.15 \text{ k}\Omega$ ) are connected in series to a battery of  $15 \text{ V}$  EMF in a circuit shown below. The key  $K_1$  has been kept closed for a long time. Then at  $t = 0$ ,  $K_1$  is opened and key  $K_2$  is closed simultaneously. At  $t = 1 \text{ ms}$ , the current in the circuit will be ( $e^5 \cong 150$ ) (2015 Main)



- (a)  $100 \text{ mA}$     (b)  $67 \text{ mA}$     (c)  $0.67 \text{ mA}$     (d)  $6.7 \text{ mA}$

Revision Series Playlist Link

<https://bit.ly/3eBbib9>

PhD Series

<https://bit.ly/3cQSxPT>

GoldMine Link

<https://bit.ly/2VhOGFF>

  
**CLICK**

